

LOGIC DESIGN

Question Bank

SOLUTION

احمد النواكل

Esmaeil

Note.

[1] - Simplify the following functions:

(a) $F(A, B, C, D) = BC + A\bar{C} + AB + BCD$

$$= (CB + \bar{C}A + BA) + BCD$$

$$= BC[1+D] + A\bar{C}$$

$$= \boxed{A\bar{C} + BC}$$

(b) $F(A, B, C, D) = BC + \bar{A} + AB + BCD$

$$= BC[\cancel{1+D}] + (\bar{A}+A)(\bar{A}+B)$$

$$= BC + \bar{A} + B$$

$$= B[\cancel{1+C}] + \bar{A}$$

$$= \boxed{\bar{A} + B}$$

(c) $F(A, B, C) = ABC + \bar{A}\underline{B}C + \bar{A}\underline{B}C + AB\bar{C} + \bar{A}\bar{B}\bar{C}$

$$= BC[\cancel{A+\bar{A}}] + \bar{A}\bar{B}[C+\bar{C}] + AB\bar{C}$$

$$= B[C+A\bar{C}] + \bar{A}\bar{B}$$

$$= B[(C+A)\cdot(C+\bar{C})] + \bar{A}\bar{B}$$

$$= \boxed{B(C+A) + \bar{A}\bar{B}}$$

(d) $F(A, B, C, D) = [(CD) + A]' + A + CD + AB$

$$= [CD \cdot \bar{A}] + A(\cancel{1+B}) + CD$$

$$= CD[\cancel{1+\bar{A}}] + A$$

$$= \boxed{A + CD}$$

Note.

$$\textcircled{2} - F(A, B, C, D) = \underline{AB} + (\underline{AB})' + \underline{ABC} + \underline{A}\bar{B}C$$

$$= AB[\cancel{1} + \cancel{C}] + (\bar{A} + \bar{B}) + \bar{A}\bar{B}C$$

$$= [AB + (\bar{A} + \bar{B})] + \bar{A}\bar{B}\cancel{C}$$

$$= AB + \bar{B} + \bar{A}(1 + \bar{B}C)$$

$$= AB + \bar{A} + \bar{B}$$

$$= \boxed{1}$$

$$\textcircled{3} - F(A, B, C, D) = (AB + \bar{A}C + BC)(\bar{B}A + \bar{B}\bar{C})$$

$$= A\underline{\bar{A}B\bar{B}} + A\underline{B\bar{B}\bar{C}} + A\underline{\bar{A}\bar{B}C} + \bar{A}\bar{B}\underline{\bar{C}\bar{C}}$$

$$= \boxed{0}$$

\textcircled{2} - Complement the following functions:

$$\textcircled{2} - F(A, B, C, D) = \bar{B}\underline{D} + \bar{A}\underline{B}\bar{C} + A\underline{CD} + \bar{A}\bar{B}C$$

$$= D[\bar{B} + AC] + \bar{A}B[\cancel{1} + \cancel{C}]$$

$$= D(\bar{B} + AC) + \bar{A}B$$

$$\therefore \bar{F} = [D(\bar{B} + AC)]' \cdot [\bar{A}B]'$$

$$= [\bar{D} + (\bar{B} + AC)] \cdot [A + \bar{B}]$$

$$= (\bar{D} + B \cdot (\bar{A} + \bar{C})) \cdot (A + \bar{B})$$

$$= (\bar{D} + \bar{A}B + BC) \cdot (A + \bar{B})$$

$$= A\bar{D} + \bar{B}\bar{D} + \underline{A}\bar{A}B + \bar{A}\bar{B}\bar{B} + A\bar{B}\bar{C} + \bar{B}\bar{B}\bar{C}$$

$$= \boxed{A\bar{D} + \bar{B}\bar{D} + A\bar{B}\bar{C}}$$

SMART FUN

Note .

b) $F(A, B, C) = A + (ABC)$

$$= A + \bar{A} + \bar{B} + \bar{C}$$
$$= 1$$

$$\therefore \bar{F} = \boxed{0}$$

c) $F(A, B, C, D) = (BC + \bar{A}D)(A\bar{B} + C\bar{D})$

$$= A\cancel{B}\cancel{B}\bar{C} + B\cancel{C}\cancel{C}\bar{D} + A\cancel{\bar{A}}\bar{B}\bar{D} + \bar{A}\cancel{C}\cancel{D}\bar{D}$$
$$= 0$$

$$\therefore \bar{F} = \boxed{1}$$

d) $F(A, B) = (AB)' + \bar{A}$

$$= \bar{A} + \bar{B} + \bar{A}$$

$$= \bar{A} + \bar{B}$$

$$\therefore \bar{F} = \boxed{AB}$$

e) $F(A, B, C, D) = (\bar{A}BC + \bar{C}D)' + (AC)'$

$$\therefore \bar{F} = [(\bar{A}BC + \bar{C}D)' + (AC)']'$$

$$= (\bar{A}BC + \bar{C}D) - (AC)$$

$$= A\cancel{\bar{A}}\cancel{B}\bar{C}C + A\cancel{C}\cancel{\bar{C}}D$$

$$= \boxed{0}$$

Note.

[3] - Convert the following functions to sum of minterms, then, what are the corresponding maxterms:

(a) $F(x, y, z) = xy + \bar{x}z$

$$= xy(z + \bar{z}) + \bar{x}z(y + \bar{y})$$

$$= xyz + xy\bar{z} + \bar{x}yz + \bar{x}\bar{y}z$$

$$\therefore \text{Sum of minterm} = M_1 + M_3 + M_6 + M_7 = \Sigma(1, 3, 6, 7)$$

$$\therefore \text{Product of maxterm} = M_0 \cdot M_2 \cdot M_4 \cdot M_5 = \Pi(0, 2, 4, 5)$$

(b) $F(A, B, C, D) = AB + \bar{B}\bar{C}D + \bar{A}\bar{B}C$

$$= AB(C + \bar{C})(A + \bar{D}) + \bar{B}\bar{C}D(A + \bar{A}) + \bar{A}\bar{B}C(D + \bar{D})$$

$$= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$+ \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$\therefore \text{Sum of minterm} = M_1 + M_2 + M_3 + M_9 + M_{12} + M_{13} + M_{14} + M_{15}$$

$$= \Sigma(1, 2, 3, 9, 12, 13, 14, 15)$$

$$\therefore \text{Product of maxterm} = M_0 \cdot M_4 \cdot M_5 \cdot M_6 \cdot M_7 \cdot M_8 \cdot M_{10} \cdot M_{11}$$

$$= \Pi(0, 4, 5, 6, 7, 8, 10, 11)$$

Note.

Q. Convert the following functions to Product of Maxterms, then what are the corresponding minterms:

$$a) F(X, Y, Z) = (\bar{X}+Y)(\bar{Y}+Z)$$

$$= [(\bar{X}+Y)+\bar{Z}\bar{Z}] \cdot [(\bar{Y}+Z)+X\bar{X}]$$

$$= (\bar{X}+Y+\bar{Z}) \cdot (\bar{X}+Y+\bar{Z}) \cdot (X+\bar{Y}+\bar{Z}) \cdot (\bar{X}+\bar{Y}+Z)$$

$$\therefore \text{Product of Maxterm} = M_2 \cdot M_4 \cdot M_5 \cdot M_6 = \Pi(2, 4, 5, 6)$$

$$\therefore \text{Sum of minterm} = M_0 + M_1 + M_3 + M_7 = \Sigma(0, 1, 3, 7)$$

$$b) F(A, B, C, D) = \bar{A}B\bar{C} + \bar{B}CD$$

$$= (\bar{A}B\bar{C} + \bar{B}) \cdot (\bar{A}B\bar{C} + C) \cdot (\bar{A}B\bar{C} + D)$$

$$= (\bar{A} + \bar{B}) \cdot (\cancel{B} + \bar{B}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + C) \cdot (B + C) \cdot (C + \bar{C})$$

$$= (\bar{A} + D) \cdot (B + D) \cdot (\bar{C} + D)$$

(موجي كيله)

$$\rightarrow (\bar{A} + \bar{B} + C\bar{C} + D\bar{D}) = (\bar{A} + \bar{B} + C + D) \cdot (\bar{A} + \bar{B} + \cancel{C} + \cancel{D}) \cdot (\bar{A} + \bar{B} + \bar{C} + \bar{D})$$

$$\rightarrow (\bar{B} + \bar{C} + A\bar{A} + D\bar{D}) = (\cancel{A} + \bar{B} + C + D) \cdot (\bar{A} + \bar{B} + \bar{C} + \bar{D}) \cdot (\bar{A} + \bar{B} + \bar{C} + D)$$

$$\rightarrow (\bar{A} + C + B\bar{B} + D\bar{D}) = (\bar{A} + B + C + D) \cdot (\cancel{A} + \cancel{B} + C + D) \cdot (\bar{A} + \bar{B} + \bar{C} + \bar{D})$$

$$\rightarrow (B + C + A\bar{A} + D\bar{D}) = (\cancel{A} + B + C + D) \cdot (\bar{A} + B + C + \bar{D}) \cdot (\bar{A} + B + C + D)$$

$$\rightarrow (\bar{A} + D + B\bar{B} + C\bar{C}) = (\bar{A} + B + C + D) \cdot (\bar{A} + B + \bar{C} + D) \cdot (\bar{A} + \bar{B} + C + D)$$

$$\rightarrow (B + D + A\bar{A} + C\bar{C}) = (\cancel{A} + B + C + D) \cdot (\bar{A} + \cancel{B} + C + D) \cdot (\bar{A} + B + \bar{C} + D)$$


$$\rightarrow (\bar{C} + D + A\bar{A} + B\bar{B}) = (\cancel{A} + B + C + D) \cdot (\bar{A} + \cancel{B} + C + D) \cdot (\bar{A} + B + \cancel{C} + D)$$

$$\therefore F = (\bar{A} + \bar{B} + C + D) \cdot (\bar{A} + \bar{B} + C + \bar{D}) \cdot (\bar{A} + \bar{B} + \bar{C} + D) \cdot (\bar{A} + \bar{B} + \bar{C} + \bar{D}) \quad \left. \begin{array}{l} \Pi(0, 1, 2, 6, 7, 8, 9, 10) \\ \bullet (\bar{A} + B + C + D) \cdot (A + B + \bar{C} + D) \cdot (\bar{A} + B + \bar{C} + D) \end{array} \right\} 12, 13, 14, 15)$$

$$\bullet (\bar{A} + B + C + \bar{D}) \cdot (A + B + C + D) \cdot (A + \bar{B} + \bar{C} + D) \cdot (A + B + C + \bar{D}) \quad \left. \begin{array}{l} \Sigma(3, 4, 5, 11) \end{array} \right\}$$

Note.

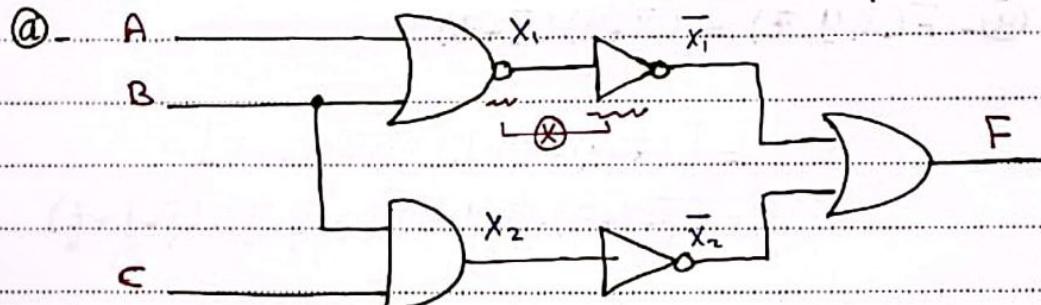5) Find the output of the following Circuits, then find the output in the simplest form, and finally find truth table:



$$X_1 = (A + B)$$

$$X_2 = B \cdot C$$

$$\bar{X}_1 = A + B$$

$$\bar{X}_2 = \bar{B} + \bar{C}$$

$$\therefore F_1 = \bar{X}_1 + \bar{X}_2 = [A + B + \bar{B} + \bar{C}] \rightarrow \text{output}$$

$$\therefore F_2 = A + (\bar{B} + \bar{B}) + \bar{C} = [1] \rightarrow \text{output (simple form)}$$

Truth table:


A	B	C	F ₁
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F_1 \equiv F_2$$

SMART FUN

Note.

(b) - A

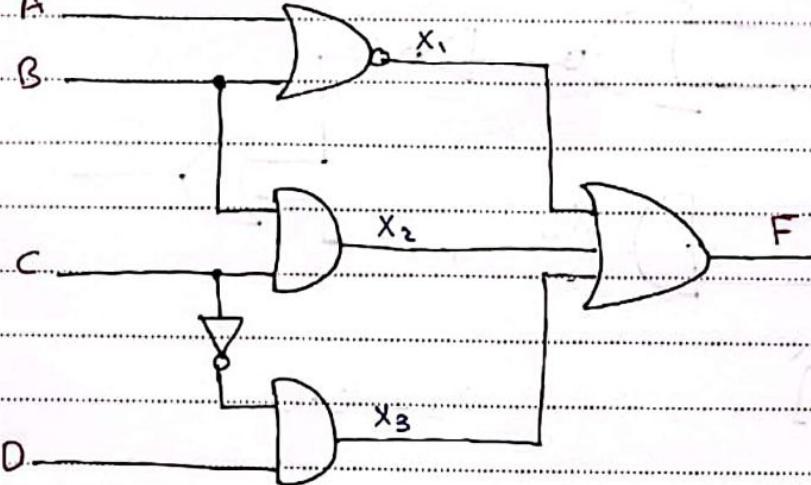

$$X_1 = (A+B)$$

$$X_2 = B \cdot C$$

$$X_3 = \bar{C} \cdot D$$

$$\therefore F_1 = [(A+B) + B \cdot C + \bar{C} \cdot D] \rightarrow \text{output}$$


$$\therefore F_2 = [\bar{A} \cdot \bar{B} + B \cdot C + \bar{C} \cdot D] \rightarrow \text{output (simple form.)}$$

Truth table:

A	B	C	D	X ₁	X ₂	X ₃	F ₁
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	1
0	0	1	0	1	0	0	1
0	0	1	1	1	0	0	1
0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	1
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	1

SMART FUN

Note.

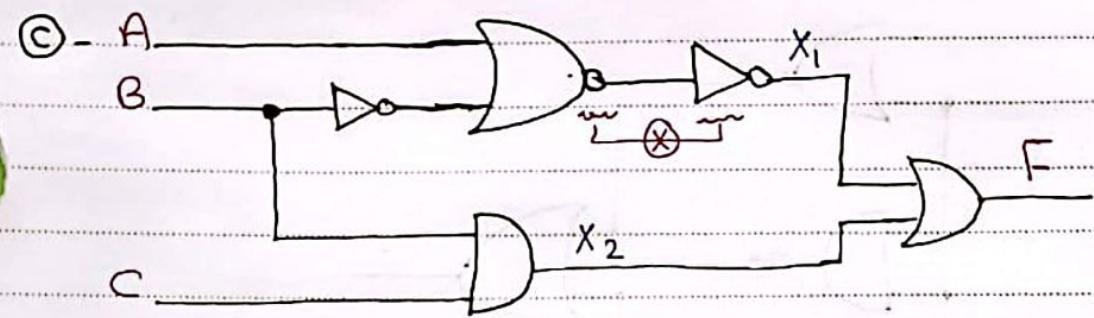

$$X_1 = [(A + \bar{B})']$$

$$X_2 = B \cdot C$$

$$X_1 = A + \bar{B}$$

$$\therefore F_1 = X_1 + X_2 = (A + \bar{B}) + B \cdot C \rightarrow \text{output}$$

$$\therefore F_2 = A + \bar{B} + C \rightarrow \text{output (Simple Form)}$$

Truth table:

A	B	C	X ₁	X ₂	F ₁	F ₂
0	0	0	1	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	0
0	1	1	0	1	1	1
1	0	0	1	0	1	1
1	0	1	1	0	1	1
1	1	0	1	0	1	1
1	1	1	1	1	1	1

$$F_1 \equiv F_2$$


SMART FUN

Note.

6 - Explain why? OTP cipher uses XOR for encryption and decryption, then, use OTP to encrypt and decrypt the letter "A" with ASCII = (65)₁₀, using the key (109)₁₀:


→ OTP cipher uses XOR, Because, "XOR" operation is reversible for example:
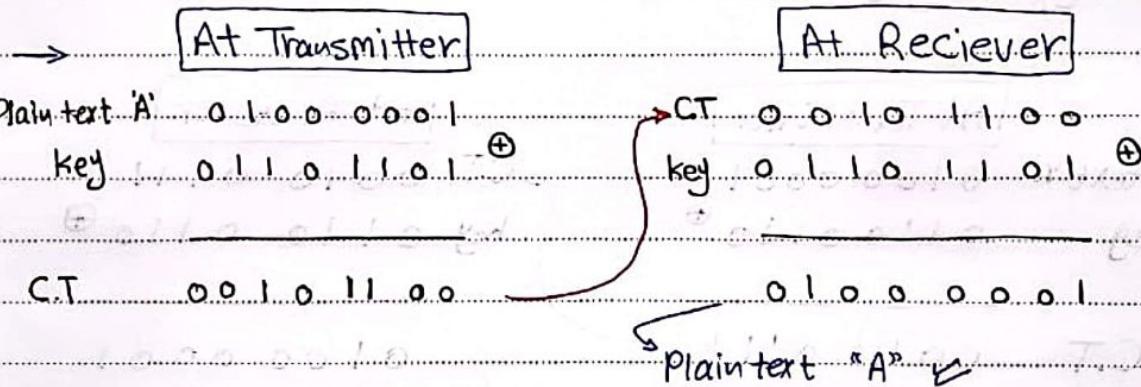
$$CT = P \oplus K \rightarrow P = CT \oplus K$$



7 - Repeat the Previous Question ~~with~~ using the following keys:


② key₁ = (143)₁₀

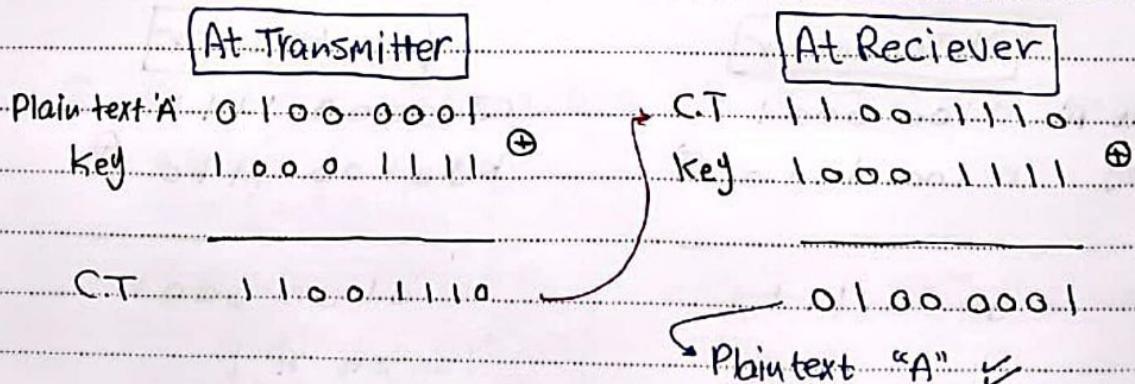


SMART FUN

Note.


⑥- $\text{key}_2 = (213)_{10}$

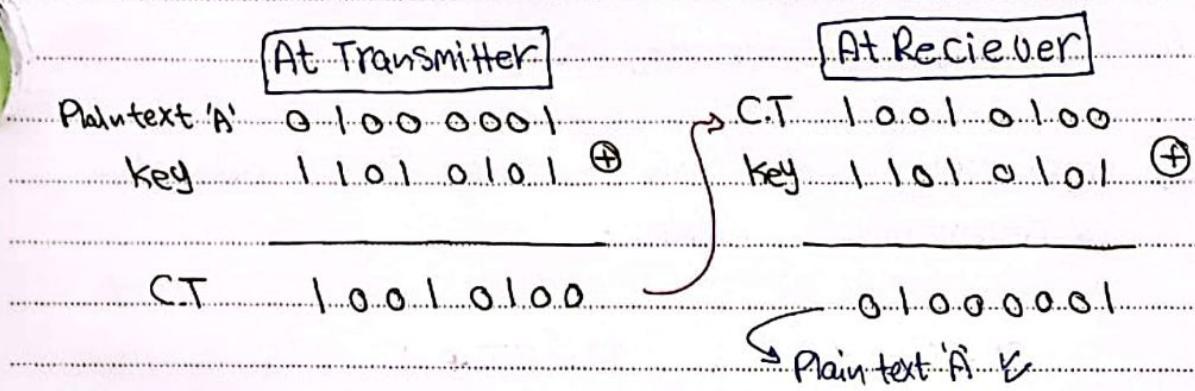

⑦- $\text{key}_3 = (102)_{10}$

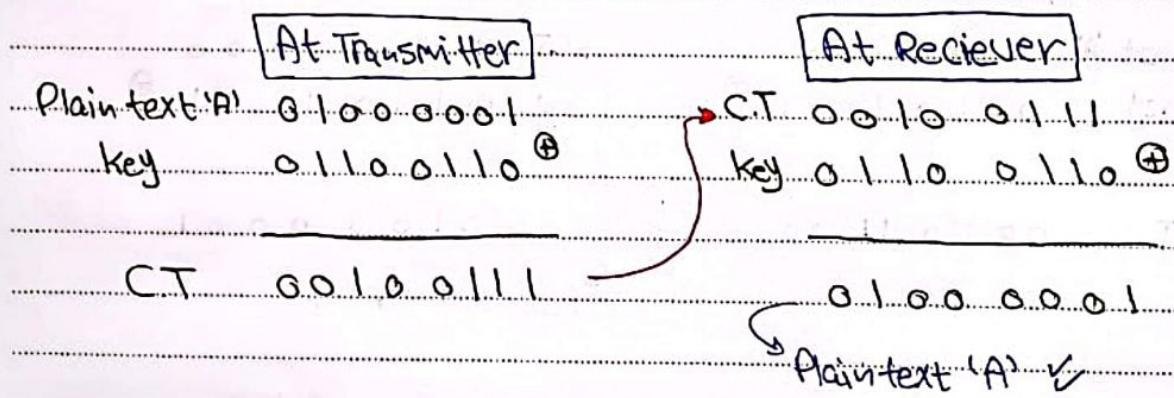

⑧- $\text{key}_4 = (78)_{10}$

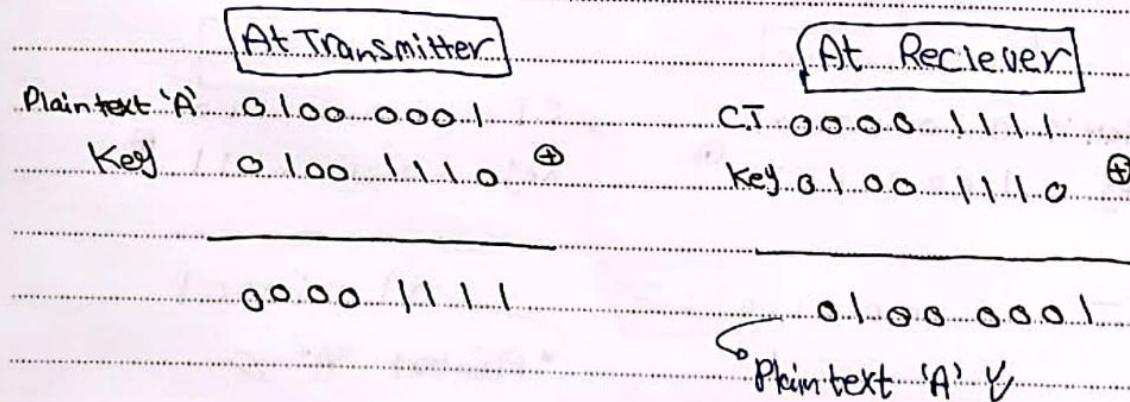

SMART FUN

Note.

8. Simplify using maps:

$$a) F(A, B, C) = A\bar{B} + BC + A\bar{B}C$$

	B	0	0	1	1
A	C	0	1	1	0
0				1	
1		1	0	1	1

$$\therefore F = BC + A\bar{B}$$

$$b) F(A, B, C, D) = \bar{A}C\bar{B} + \bar{A}\bar{D} + C\bar{D}B + \bar{A}B\bar{C}$$

	C	0	0	1	1
A	B	D	0	1	1
0	0	1	1	1	1
0	1	1	1	1	1
1	1			1	
1	0				

$$\therefore F = \bar{A}\bar{D} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + BC\bar{D}$$

$$c) F(x, y, z) = \Pi(0, 1, 3, 4, 5)$$

	y	0	0	1	1
x	z	0	1	1	0
0	0	0	0	0	1
1	0	0	1	1	1

$$\therefore F = xy + y\bar{z}$$

$$d) F(A, B, C, D) = \Pi(0, 3, 4, 6, 7, 9, 11, 12, 13)$$

	C	0	0	1	1	1
A	B	D	0	1	0	1
0	0	0	1	0	1	1
0	1	0	1	0	0	0
1	1	0	0	1	1	1
1	0	0	0	0	0	1

$$\therefore F = \bar{A}\bar{C}D + ABC + \bar{B}CD + A\bar{B}\bar{D}$$

Note.

$$\textcircled{Q} - F(A, B, C) = \sum(0, 1, 2, 4, 6)$$

	B	0	0	1	1
A	C	0	1	1	0
0		m_0	m_1	m_3	m_2
1		m_4	m_5	m_2	m_6
		1	1	1	1

$$\therefore F = \bar{C} + \bar{A}\bar{B}$$

$$\textcircled{P} - F(A, B, C, D) = \sum(1, 2, 4, 5, 6, 7, 8, 12, 13, 15)$$

	C	0	0	1	1
A	D	0	1	1	0
0	0	m_0	m_1	m_3	m_2
0	1	m_4	m_5	m_2	m_6
1	1	m_{12}	m_{13}	m_{15}	m_{14}
1	0	m_8	m_9	m_{11}	m_{10}

$$\therefore F = BD + \bar{A}B + \bar{A}\bar{C}D + \bar{A}C\bar{D} + A\bar{C}\bar{D}$$

\textcircled{Q}

	C	0	0	1	1
A	B	0	1	1	0
0	0	0	0	1	
0	1	1	0	0	1
1	1	1	0	1	1
1	0	1	0	1	1

	C	0	0	1	1
A	B	0	1	0	0
0	0	1	0	0	1
0	1	1	1	1	1
1	1	0	1	1	0
1	0	0	0	1	1

$$\therefore F = \bar{C}\bar{D} + AC + A\bar{D} + B\bar{C}\bar{D}$$

$$\therefore F = \bar{A}B + BD + \bar{B}\bar{D}$$

	C	0	0	1	1
A	B	0	1	1	0
0	0	1	0	1	
0	1	1	1	0	1
1	1	1	X	1	1
1	0	1	0	0	1

$$\therefore F = \bar{D} + AB + BC$$

	C	0	0	1	1
A	B	0	1	0	1
0	0	1	0	1	
0	1	0	0	1	0
1	1	X	X	1	1
1	0	X	0	1	X

$$\therefore F = AB + CD + \bar{B}\bar{D}$$

SMART FUN

Note .

	C	O	O	I	I
A	B	D	O	I	O
0	0	0	1	1	1
0	1	0	X	1	1
1	1	1	0	1	X
1	0	0	0	0	0

$$\therefore F = CD + \bar{A}C + \bar{A}D + AB\bar{D}$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	0	1	0	1
0	1	0	1	0	1
1	1	X	0	1	0
1	0	0	X	0	1

$$\therefore F = A\oplus B \oplus C \oplus D$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	1	0	0	1
0	1	1	0	0	X
1	1	1	1	1	1
1	0	X	1	1	1

$$\therefore F = A + \bar{B}$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	1	0	0	1
0	1	1	0	0	1
1	1	1	X	0	0
1	0	X	X	0	0

$$\therefore F = \bar{C}\bar{D} + \bar{A}\bar{D}'$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	1	0	1	1
0	1	0	1	1	1
1	1	0	0	X	X
1	0	X	1	1	1

$$\therefore F = AB + \bar{B}\bar{D} + BC + \bar{A}\bar{C}D$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	0	1	0	1
0	1	1	0	1	0
1	1	0	1	X	1
1	0	1	0	1	0

$$\therefore F = A \oplus B \oplus C \oplus D$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	1	0	0	1
0	1	1	X	0	0
1	1	1	X	0	0
1	0	X	0	0	1

$$\therefore F = \bar{C}\bar{D} + \bar{B}\bar{D}$$

	C	O	O	I	I
A	B	D	O	I	O
0	0	0	1	1	X
0	1	0	0	1	0
1	1	1	X	0	0
1	0	1	1	1	D

$$\therefore F = AB + AC + \bar{A}CD + \bar{B}\bar{D}$$

SMART FUN

Note.

	C D	0	0	1	1
A B	0	1	1	0	
0 0	1	X	0	0	
0 1	0	1	X	0	
1 1	0	0	1	X	
1 0	0	0	0	1	

$$\therefore F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + A\bar{C}\bar{D}$$

	C D	0	0	1	1
A B	0	1	0	1	
0 0	0	0	0	X	0
0 1	0	0	X	1	0
1 1	X	1	0	0	X
1 0	0	0	0	1	1

$$\therefore F = A\bar{B}\bar{C} + B\bar{C}\bar{D} + \bar{A}BD$$

	C D	0	0	1	1
A B	0	0	1	1	0
0 0	1	1	1	1	0
0 1	X	X	0	0	
1 1	X	X	0	0	
1 0	D	0	1	1	

$$\therefore F = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{B}C$$

	C D	0	0	1	1
A B	0	1	1	X	1
0 0	0	1	1	X	1
0 1	1	0	0	0	1
1 1	1	1	X	1	1
1 0	1	1	1	1	1

$$\therefore F = A + \bar{B} + \bar{B}$$

	C D	0	0	1	1
A B	0	0	1	1	0
0 1	0	1	1	1	1
1 1	0	X	1	0	
1 0	0	1	1	1	

$$\therefore F = D + A\bar{B}C + \bar{A}BC$$

	C D	0	0	1	1
A B	0	0	0	X	1
0 1	X	0	0	0	1
1 1	1	0	1	1	1
1 0	0	X	1	0	

$$\therefore F = B\bar{D} + ABC + \bar{B}D$$

Note.

	C D	0	0	1	1
A B	0	1	1	0	
0 0	1	X	0	0	
0 1	0	1	X	0	
1 1	0	0	1	X	
1 0	0	0	0	1	

$$\therefore F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + A\bar{C}\bar{D}$$

	C D	0	0	1	1
A B	0	1	0	1	
0 0	0	0	0	X	0
0 1	0	0	X	1	0
1 1	X	1	0	0	X
1 0	0	0	0	1	1

$$\therefore F = A\bar{B}\bar{C} + B\bar{C}\bar{D} + \bar{A}BD$$

	C D	0	0	1	1
A B	0	0	1	1	0
0 0	1	1	1	1	0
0 1	X	X	0	0	
1 1	X	X	0	0	
1 0	D	0	1	1	

$$\therefore F = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{B}C$$

	C D	0	0	1	1
A B	0	1	1	1	0
0 0	1	1	X	1	0
0 1	1	0	0	0	1
1 1	1	1	X	1	1
1 0	1	1	1	1	1

$$\therefore F = A + \bar{B} + \bar{B}$$

	C D	0	0	1	1
A B	0	0	1	1	0
0 1	0	1	1	1	1
1 1	0	X	1	0	
1 0	0	1	1	1	

$$\therefore F = D + A\bar{B}C + \bar{A}BC$$

	C D	0	0	1	1	
A B	0	0	0	X	1	0
0 1	X	0	0	0	1	1
1 1	1	0	1	1	1	1
1 0	0	X	1	0	0	

$$\therefore F = B\bar{D} + ABC + \bar{B}D$$

Note.

Q - Simplify the following using Maps twice : In sum of Product form. Then In Product of sums form :

a) $F(A, B, C, D) = \sum(3, 4, 6, 7, 9, 10, 13, 15)$

	C	0	0	1	1
	A	B	0	1	1
0	0	0	0	1	0
0	1	0	0	1	1
1	0	0	1	1	0
1	0	1	0	1	1

$$\therefore F_1 = \bar{A}CD + \bar{A}B\bar{D} + ABD + A\bar{C}D + A\bar{B}C\bar{D}$$

$$\therefore F_2 = (A+C+\bar{D})(A+B+D)(\bar{A}+\bar{B}+D)$$

$$(\bar{A}+C+D)(\bar{A}+B+\bar{C}+\bar{D})$$

b) $F(A, B, C, D) = \bar{A}B\bar{C} + A\bar{C} + BD + \bar{A}$

	C	0	0	1	1
	A	B	0	1	1
0	0	1	1	1	1
0	1	1	1	1	1
1	1	1	1	1	0
1	0	1	1	0	0

$$\therefore F_1 = \bar{A} + \bar{C} + BD$$

$$\therefore F_2 = (\bar{A}+B+\bar{C})(\bar{A}+\bar{C}+D)$$

c) $F(A, B, C, D) = \prod(1, 3, 7, 9, 11, 13, 14)$

	C	0	0	1	1
	A	B	0	1	1
0	0	1	0	1	0
0	1	1	1	0	1
1	1	1	0	1	1
1	0	1	0	0	1

$$\therefore F_1 = \bar{C}\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{D} + \bar{A}B\bar{C} + ABCD$$

$$\therefore F_2 = (B+\bar{D})(\bar{A}+C+\bar{D})(A+\bar{C}+\bar{D})$$


$$(\bar{A}+\bar{B}+\bar{C}+D)$$

Note .

1 / 1


10. Draw the following function $F(x,y,z) = xy + \bar{x}\bar{y} + \bar{y}z$, using:

a. AND, OR, and NOT gates:

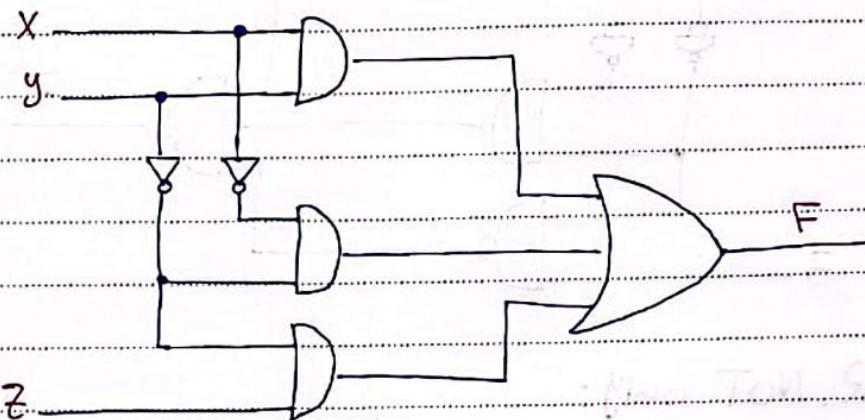

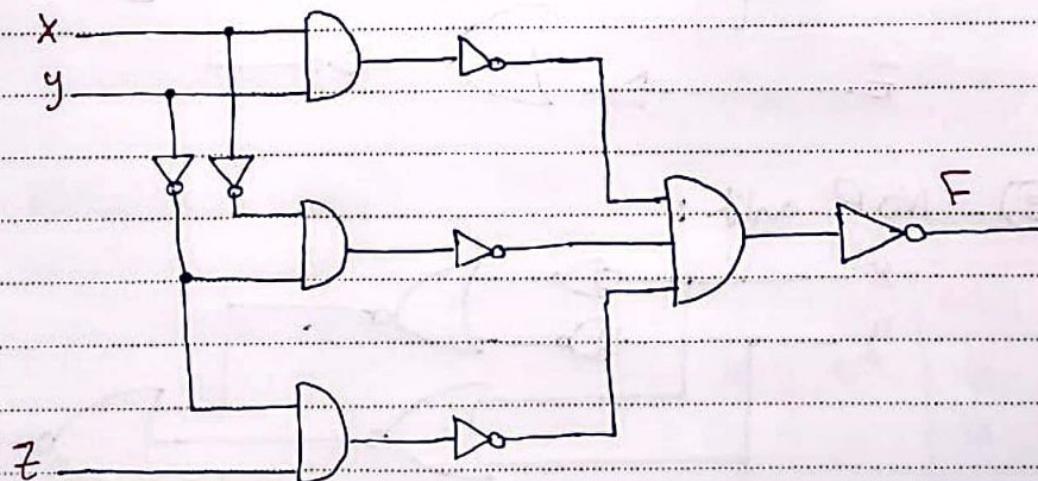
b. AND, NOT only:

$$\begin{aligned} F &= [xy + \bar{x}\bar{y} + \bar{y}z]'' \\ &= [(xy)'' (\bar{x}\bar{y})'' (\bar{y}z)''] \end{aligned}$$




Note.

③ - NAND only:

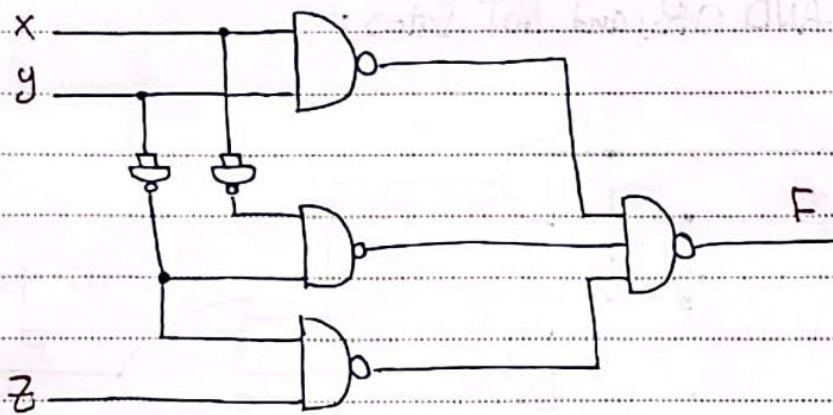


④ - OR, NOT only:
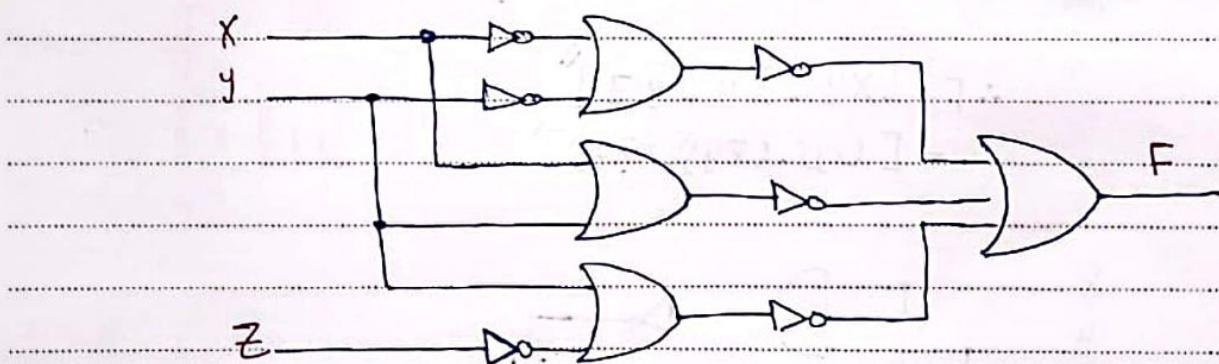
$$\begin{aligned} \therefore F &= (xy)'' + (\bar{x}\bar{y})'' + (\bar{y}z)'' \\ &= (\bar{x} + \bar{y})' + (x + y)' + (y + \bar{z})' \end{aligned}$$



⑤ - NOR only:

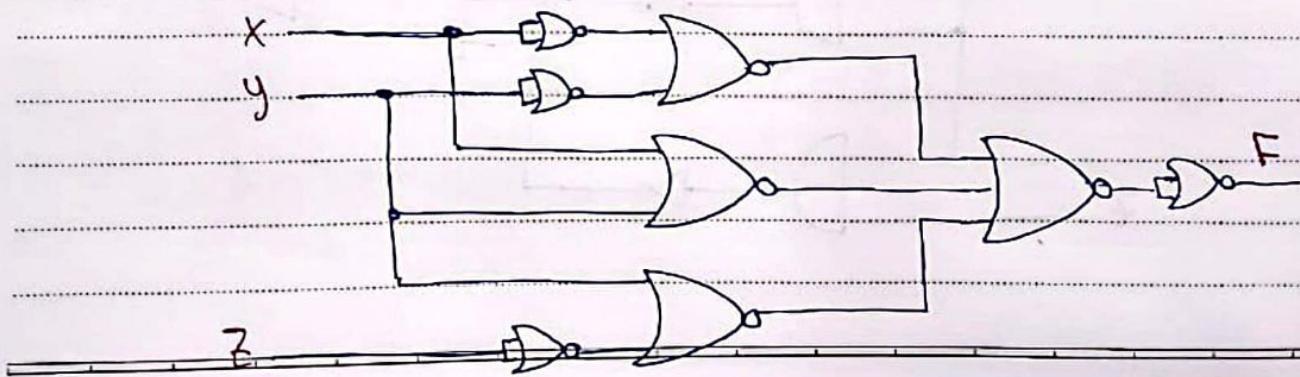

SMART FUN

Note .

11 - State, then Prove:

a) De-Morgan laws:

$$\rightarrow (x+y)' = \bar{x}\bar{y}$$

$$\rightarrow (xy)' = \bar{x} + \bar{y}$$

x	y	L.H.S	R.H.S
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

$$\begin{matrix} \leftarrow \\ \textcircled{=} \\ \rightarrow \end{matrix}$$

x	y	L.H.S	R.H.S
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

$$\begin{matrix} \leftarrow \\ \textcircled{=} \\ \rightarrow \end{matrix}$$

b) Distribution laws:

$$\rightarrow x.(y+z) = xy + xz$$

x	y	z	L.H.S	R.H.S
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

$$\begin{matrix} \leftarrow \\ \textcircled{=} \\ \rightarrow \end{matrix}$$

c) Absorption laws:

$$\rightarrow x+xy = x(1+y) = x$$

x	y	L.H.S	R.H.S
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	1

$$\begin{matrix} \leftarrow \\ \textcircled{=} \\ \rightarrow \end{matrix}$$

Question 9 simplfy using maps

a. $F(A,B,C,D) = \sum(3,4,6,7,9,10,13,15)$.

		C 0	0	1	1
	D 0	1	1	1	0
A	0	0	0	1	1
B	0	0	1	1	1
0	1	1	0	1	1
1	1	0	1	1	0
1	0	1	1	0	1

$$F(A, B, C, D) = A\bar{B}C\bar{D} + A\bar{C}D + A\bar{B}D + \bar{A}\bar{B}\bar{D} + \bar{A}CD$$

$$F(A, B, C, D) = (A+B+D) \cdot (A+C+\bar{D}) \cdot (\bar{A}+\bar{B}+D) \cdot (\bar{A}+C+D) \cdot (\bar{A}+B+\bar{C}+\bar{D})$$

b. $F(A,B,C,D) = A'BC' + AC' + \underline{BD} + A'$

		C 0	0	1	1
	D 0	1	1	1	0
A	0	1	1	1	1
B	0	1	1	1	1
0	1	1	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0

$$F(A, B, C, D) = \bar{A} + \bar{C} + BD \leftarrow \text{sum of product}$$

$$F(A, B, C, D) = (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{C} + D) \leftarrow \text{product of sums}$$


c. $F(A,B,C,D) = \prod(1,3,,7,9,11,13,14)$.

		C 0	0	1	1
	D 0	1	1	1	0
A	0	1	1	1	1
B	0	1	1	1	1
0	1	1	1	1	1
1	1	1	0	1	1
1	0	1	1	0	1

$$F(A, B, C, D) = \bar{C}\bar{D} + \bar{B}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{D} + A\bar{B}CD$$

$$F(A, B, C, D) = (B+\bar{D}) \cdot (A+\bar{C}+\bar{D}) \cdot (\bar{A}+C+\bar{D}) \cdot (\bar{A}+\bar{B}+\bar{C}+D)$$

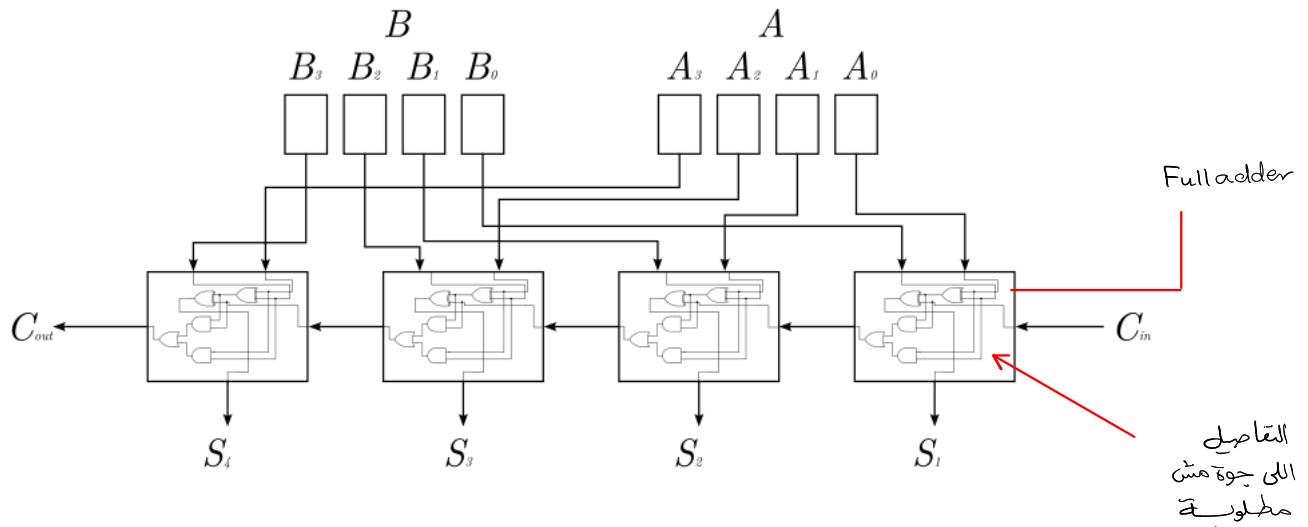12. Draw 4-bit parallel adder, then show how to convert it to parallel subtractor.




by implementing the equation that says

$$A - B = A + \overline{B} + 1$$

we can transform it into a 4-bit subtractor by using a Not gate with B inputs assuming A bigger than B and changing the Cin from 0 to 1

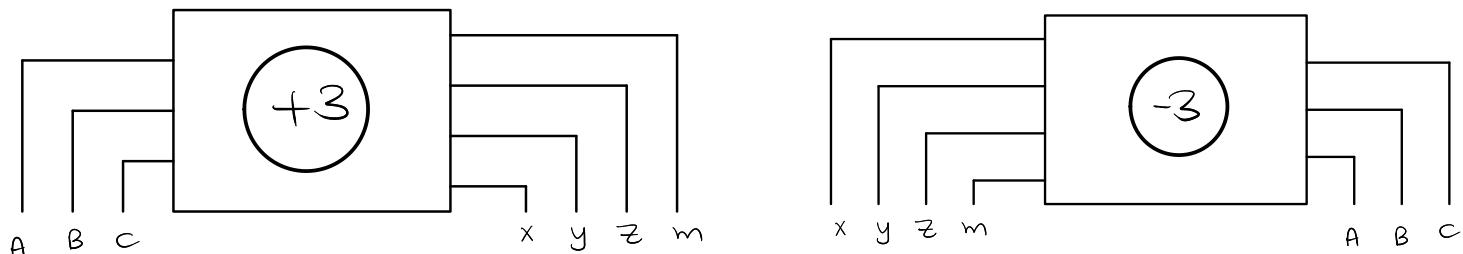13. Implement Excess-3 code to encrypt 3 bit number in both transmitter and receiver sides.



at Transmitter

	C	B	O	1	1	0
A	1	0	1	1	0	0
O	0	1	1	1	0	0
I	1	0	0	0	0	0

$$m = \bar{C}$$

$$z = \bar{B}\bar{C} + BC$$

	C	B	O	1	1	0
A	0	1	1	1	1	0
O	0	1	0	0	0	0
I	1	0	0	0	0	0


$$y = \bar{A}C + \bar{A}B + A\bar{B}C$$

$$\bar{A}(B+C) + A \cdot (\bar{B}C)$$

	C	B	O	1	1	0
A	0	0	0	0	0	0
O	0	1	1	1	1	0
I	0	1	1	1	1	0

$$x = AC + AB$$

A	B	C	X	Y	Z	m̄
0	0	0	0	0	1	1
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	1	1
1	0	1	1	0	0	0
1	1	0	1	0	0	1
1	1	1	1	0	1	0

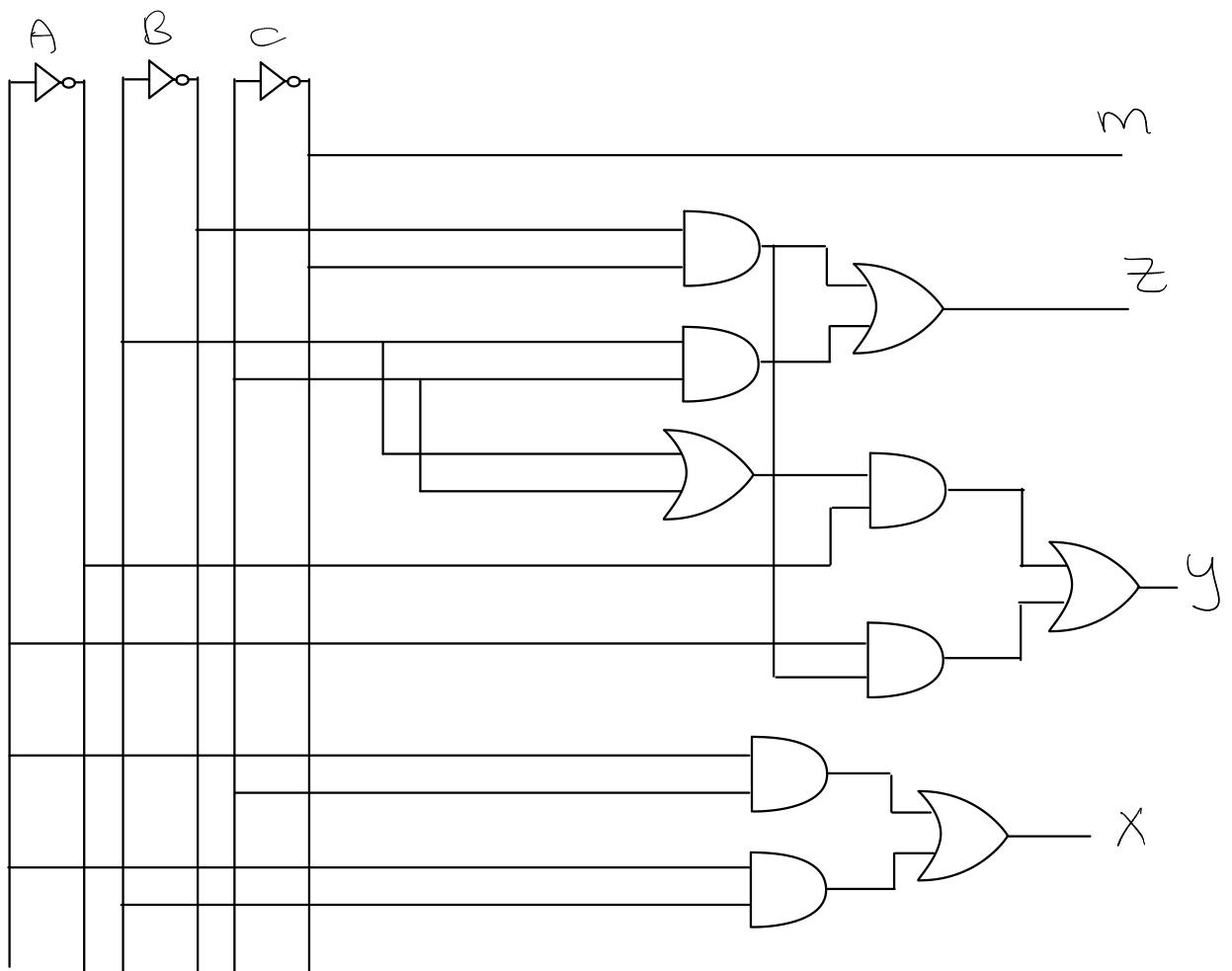

at receiver

$$C = \bar{m}$$



	x	y	z	m	C
x	0	0	0	0	0
y	0	0	0	0	0
z	0	0	0	0	0
m	0	0	0	0	0
C	0	0	0	0	0

$$B = \bar{z}m + \bar{m}z = z \oplus m$$

	x	y	z	m	B
x	0	0	0	0	0
y	0	0	0	0	0
z	0	0	0	0	0
m	0	0	0	0	0
B	0	0	0	0	0

$$A = x + yzm$$


x	y	z	m	A	B	C
0	0	0	0	X	X	X
0	0	0	1	X	X	X
0	0	1	0	X	X	X
0	0	1	1	0	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	1	0	1
1	0	0	1	1	1	0
1	0	1	0	1	1	1
1	0	1	1	X	X	X
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

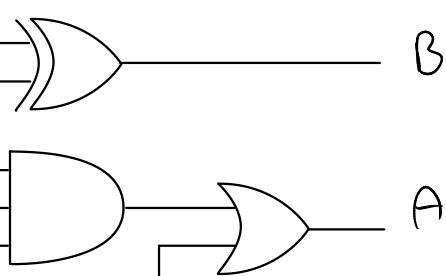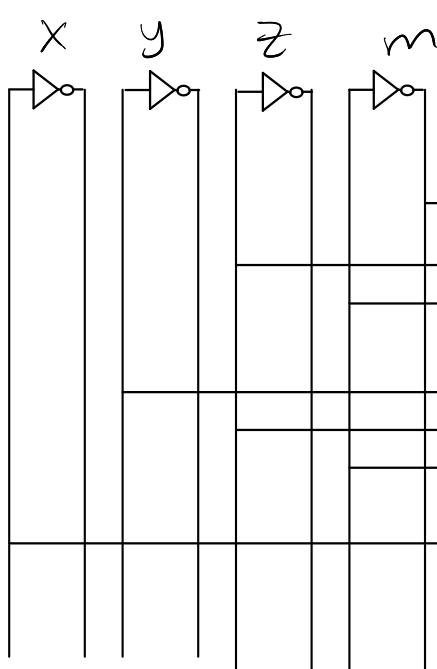

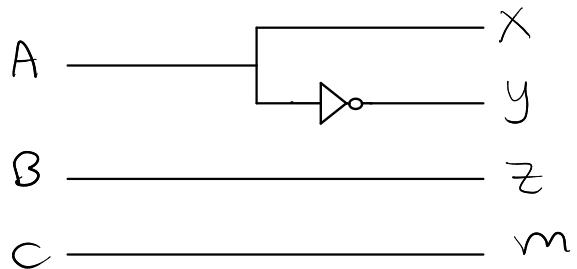14. Implement Excess-4 code to encrypt 3 bit number in both transmitter and receiver sides.

at Transmitter


$$m = c \quad z = \bar{B} \quad y = \bar{A} \quad x = A$$



A	B	C	X	y	z	m
0	0	0	0	1	0	0
0	0	1	0	1	0	1
0	1	0	0	1	1	0
0	1	1	0	1	1	1
1	0	0	1	0	0	0
1	0	1	1	0	0	1
1	1	0	1	0	1	0
1	1	1	1	0	1	1

at receiver


$$c = m \quad B = z \quad A = \bar{y}$$

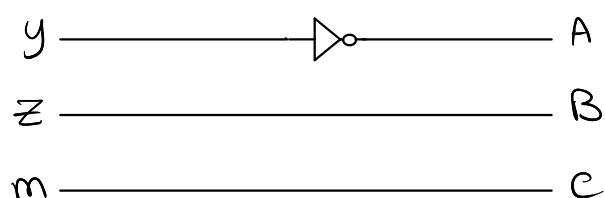

x	y	z	m	a	b	c
0	0	0	0	X	X	X
0	0	0	1	X	X	X
0	0	1	0	X	X	X
0	0	1	1	X	X	X
0	1	0	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	1
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

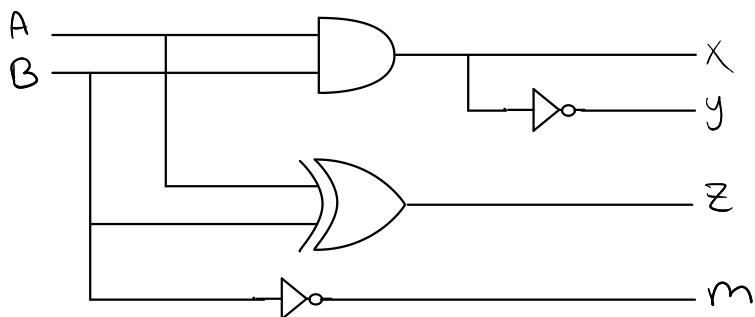
15. Implement Excess-5 code to encrypt 2 bit number in both transmitter and receiver sides.

$$m = \overline{B} \quad z = A \oplus B \quad y = (A \oplus B) \quad x = AB$$



A	B	X	Y	Z	m
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	1	1
1	1	1	0	0	0
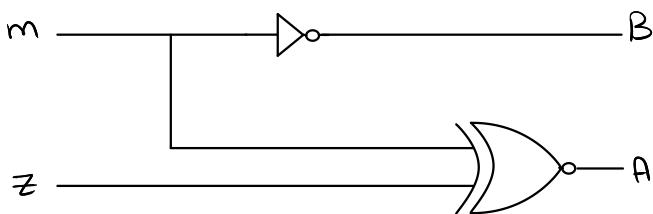
$$B = \overline{m} \quad A = \overline{z} \odot m$$



X	Y	Z	m	A	B
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	1	1

حَمْلَةٌ عَلَى سُورَةِ

16. Implement Excess-2 code to encrypt BCD number (0→9) in both transmitter and receiver side.

$$D = m \quad C = \bar{z}$$


	x	y	z	m	D
m	0	0	0	0	0
z	0	0	1	1	0
y	0	1	1	0	0
x	1	1	X	X	0
	1	0	0	0	1
	0	1	0	1	1
	1	0	1	1	1

$$B = y\bar{z} + \bar{y}z = z \oplus y$$

	x	y	z	m	D
m	0	0	0	0	0
z	0	0	1	1	0
y	0	1	X	X	0
x	1	1	X	X	0
	1	1	0	0	1
	0	1	1	1	1
	1	0	0	0	1
	1	0	0	1	1
	1	0	1	0	1
	1	1	0	0	0

$$A = x + yz$$

x	y	z	m	A	B	C	D
0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	1
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	1	0
1	0	0	1	1	0	1	1
1	0	1	0	X	X	X	0
1	0	1	1	X	X	X	1
1	1	0	0	X	X	X	0
1	1	0	1	X	X	X	1
1	1	1	0	X	X	X	0
1	1	1	1	X	X	X	1

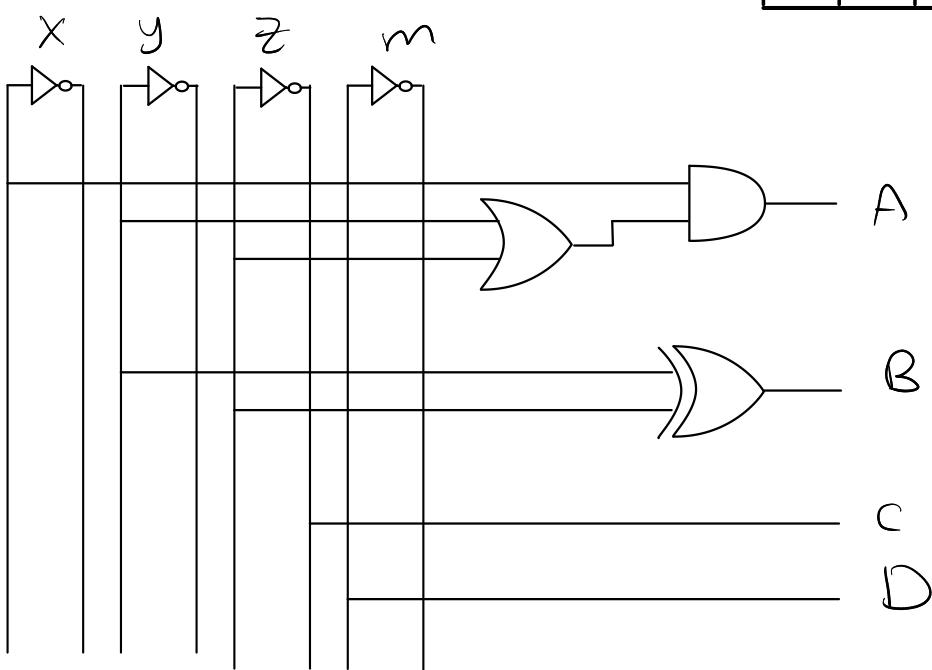

$$m=D \quad z=\bar{c}$$


AB		00	01	11
0	0	X	X	0
0	1	0	0	1
1	1	X	X	X
1	0	1	1	0

$$y = \overline{B}\overline{C} + BC = B \odot C$$

		C	0	0	(1)
	D	0	1	1	0
A	B	X	0X	0	0
0	0	0	0	0	0
0	1	X	X	X	X
1	1	0	0	1	1


$$X = AC$$

A	B	C	D	X	Y	Z	m
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	1
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	0	1	1	0
1	0	0	1	0	1	1	1
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	1
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	(1	1	X	X	X)

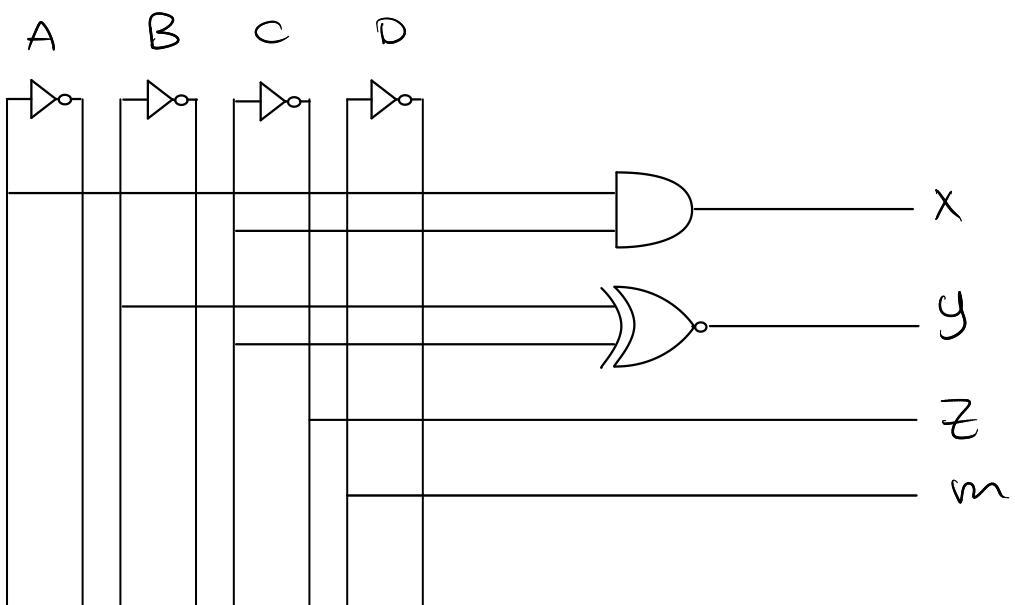

17. Design:

a. Full Adder circuit.

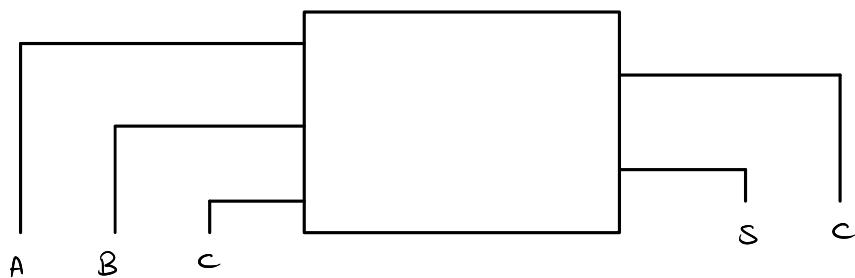


	B	G	O	C	1
A	0	1	1	0	0
C	0	0	1	0	1
1	1	0	1	0	0

$$S = A \oplus B \oplus C$$


	B	G	O	C	1
A	0	0	1	0	0
C	0	0	0	1	1
1	0	0	0	1	0

$$C_{out} = BC + AC + AB$$

A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

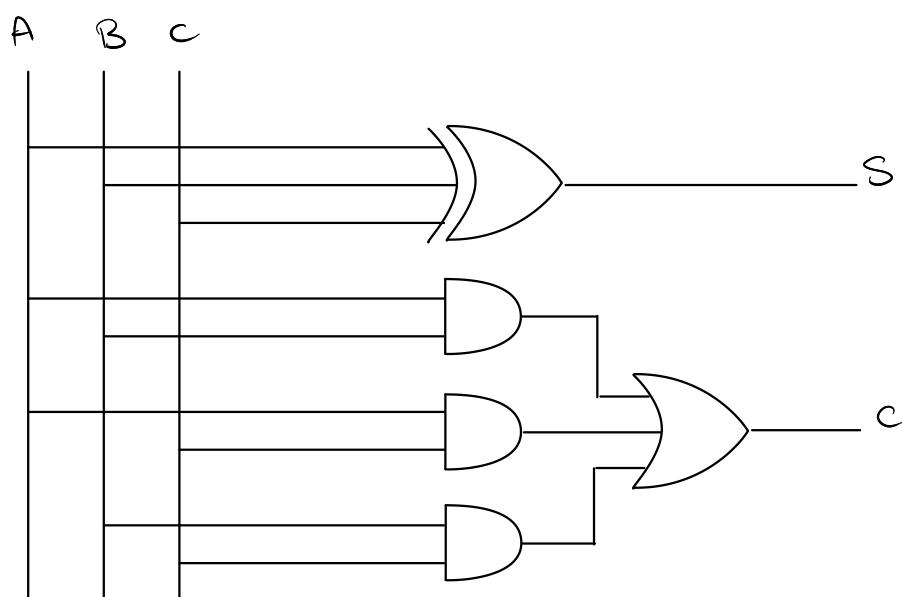

b. Full Subtractor circuit.

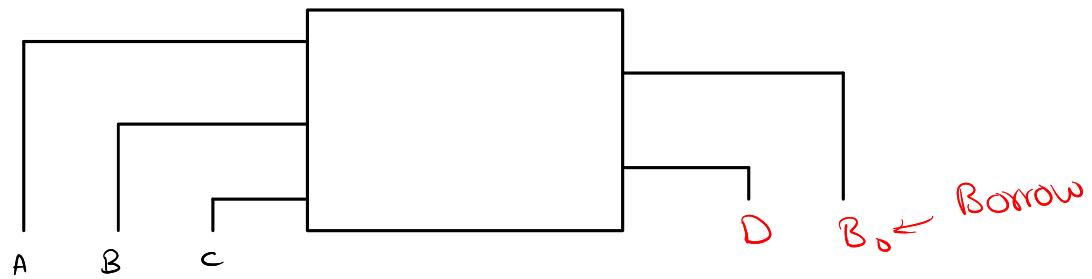


	B	G	O	C	D
A	/	/	/	/	
0	0	1	0	1	
1	1	0	1	0	

$$D = A \oplus B \oplus C$$

	B	G	O	C	D
A	/	/	/	/	
0	0	1	0	1	
1	0	0	1	0	

$$B_o = \bar{A}C + BC + \bar{A}B$$


A	B	C	D	B _o
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

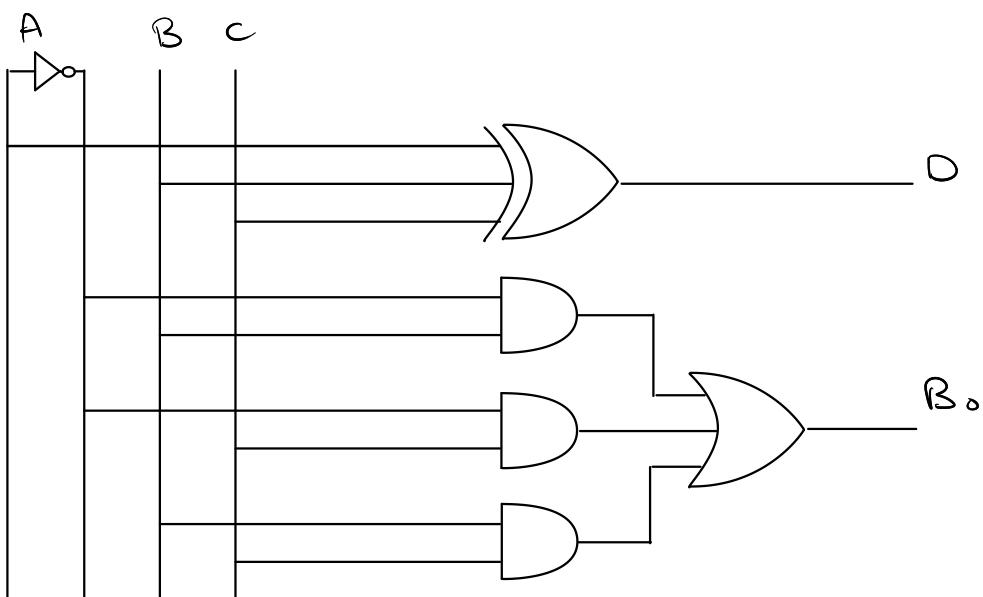

if you want
to understand
Truth ↓ table




c. 2X4 decoder.

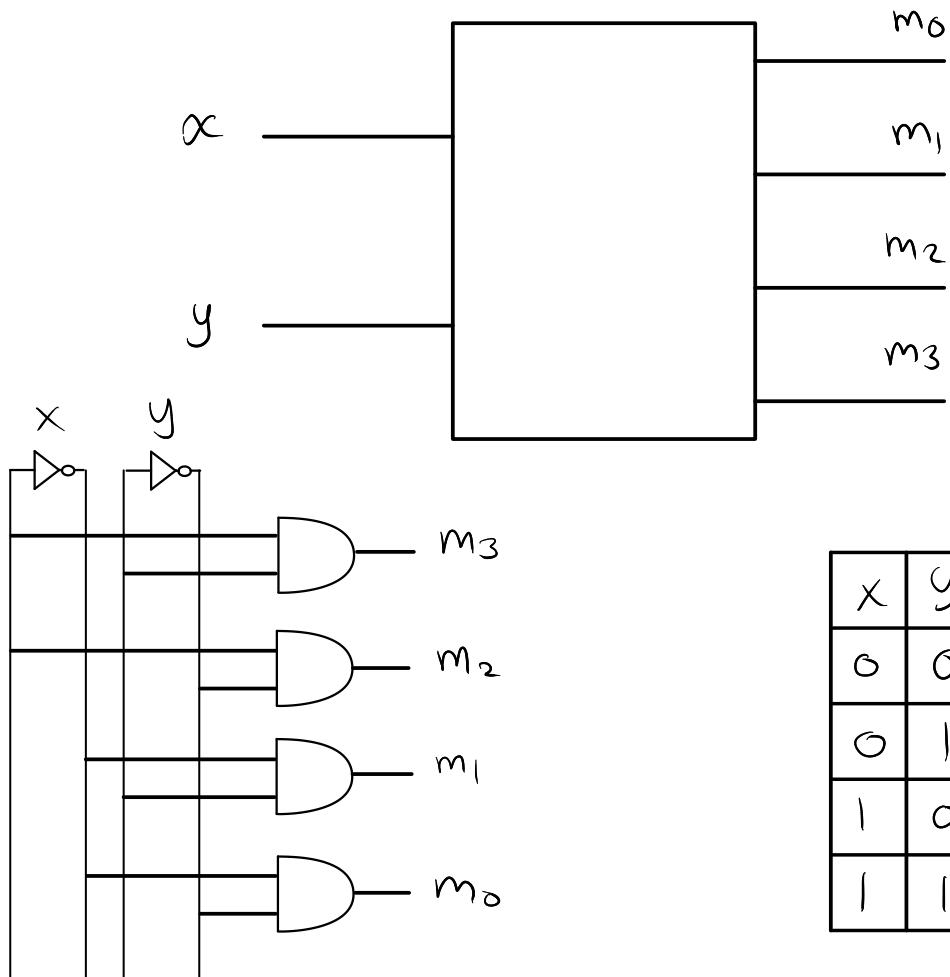


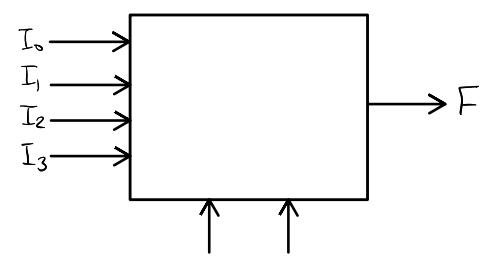d. 4X1 Multiplexer.


$$F = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$



S_1	S_0	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

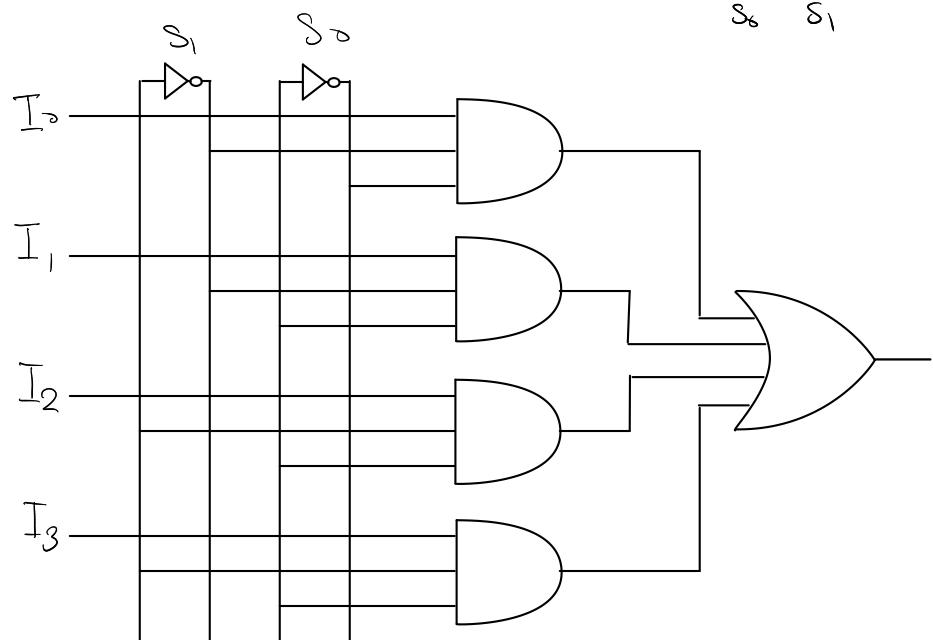


e. 1X2 Demultiplexer.

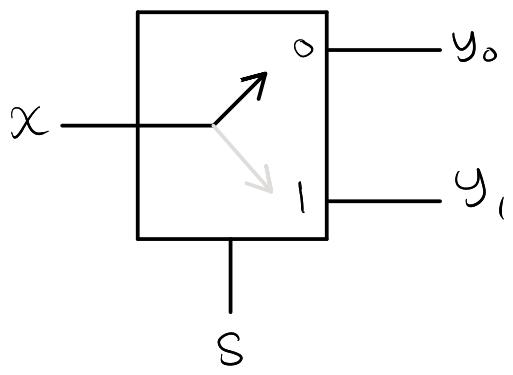


S	y ₁	y ₀
0	0	X
1	X	0

$$y_1 = SX$$

$$y_0 = \bar{S}X$$

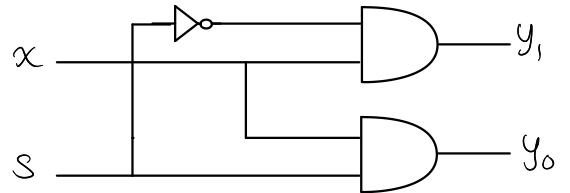

f. 1X4 Demultiplexer.

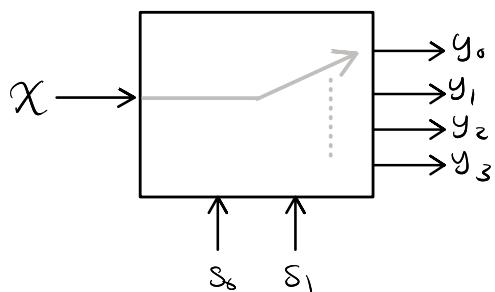


S ₁	S ₀	y ₃	y ₂	y ₁	y ₀
0	0	0	0	0	X
0	1	0	0	X	0
1	0	0	X	0	0
1	1	X	0	0	0

$$y_3 = S_1 S_0 X$$


$$y_2 = S_1 \bar{S}_0 X$$

$$y_1 = \bar{S}_1 S_0 X$$

$$y_0 = \bar{S}_1 \bar{S}_0 X$$

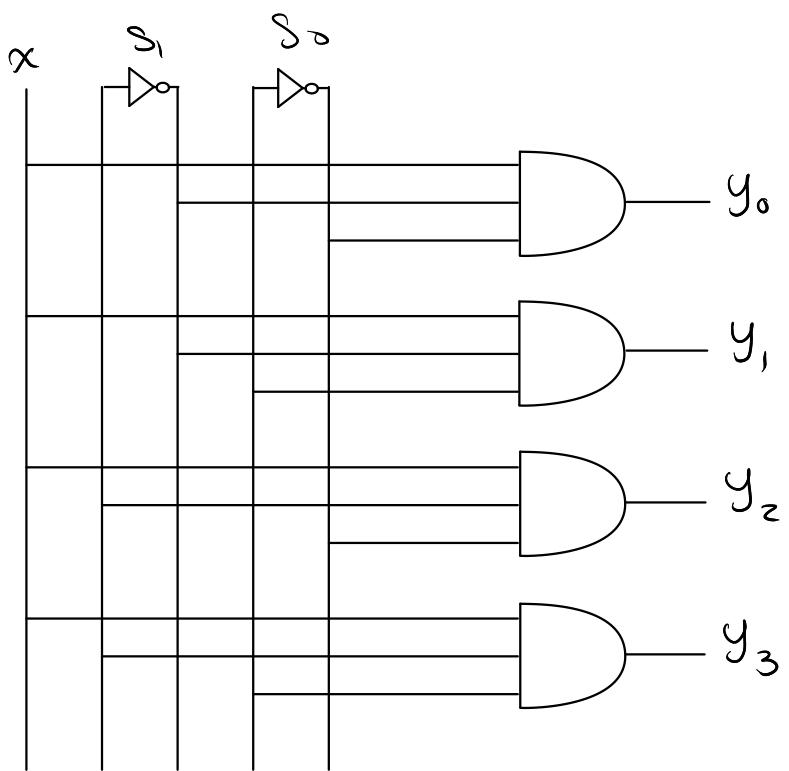


g. 4X2 Encoder.

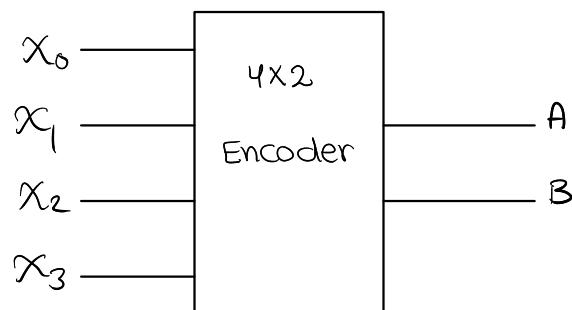


X_3	X_2	X_1	X_0	A	B
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$A = X_2 + X_3$$

$$B = X_1 + X_3$$

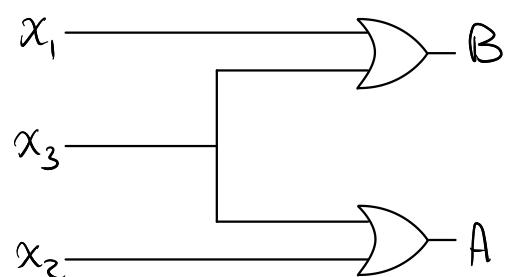

h. 2-bit Comparator.

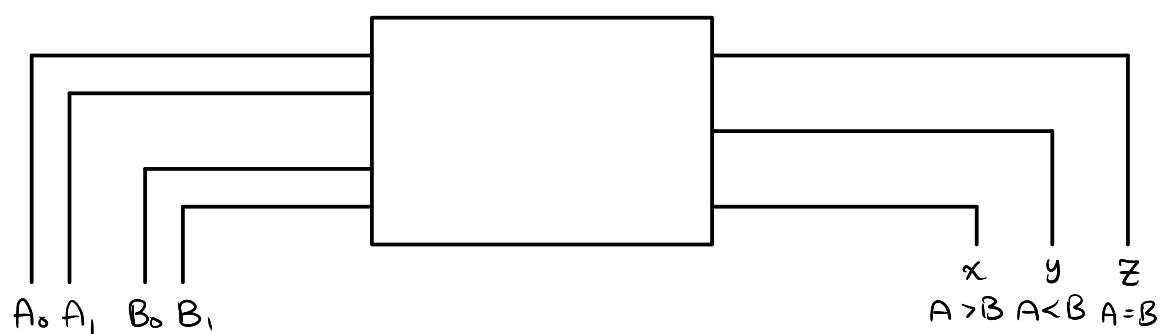

A_1	A_0	B_1	B_0	X	Y	Z
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	1	0	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	1

$B_1 \quad 0 \quad 0 \quad | \quad 1 \quad 1$
 $B_0 \quad 0 \quad 1 \quad | \quad 1 \quad 0$

A_1	A_0	0	0	0	0
0	0	0	0	0	0
0	1	0	0	0	0
1	1	1	0	0	1
1	1	1	1	0	0

$$X = A_1 \bar{B}_1 + A_1 A_0 \bar{B}_0 + A_0 \bar{B}_1 \bar{B}_0$$

$B_1 \quad 0 \quad 0 \quad | \quad 1 \quad 1$
 $B_0 \quad 0 \quad 1 \quad | \quad 1 \quad 0$


A_1	A_0	0	1	1	1
0	0	0	0	1	1
0	1	0	0	0	0
1	1	0	0	0	0
1	1	0	1	0	0

$$Y = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + A_0 B_1 B_0$$

$B_1 \quad 0 \quad 0 \quad | \quad 1 \quad 1$
 $B_0 \quad 0 \quad 1 \quad | \quad 1 \quad 0$


A_1	A_0	1	0	0	0
0	0	0	1	0	0
0	1	0	0	1	0
1	1	0	0	0	1
1	1	0	0	0	1
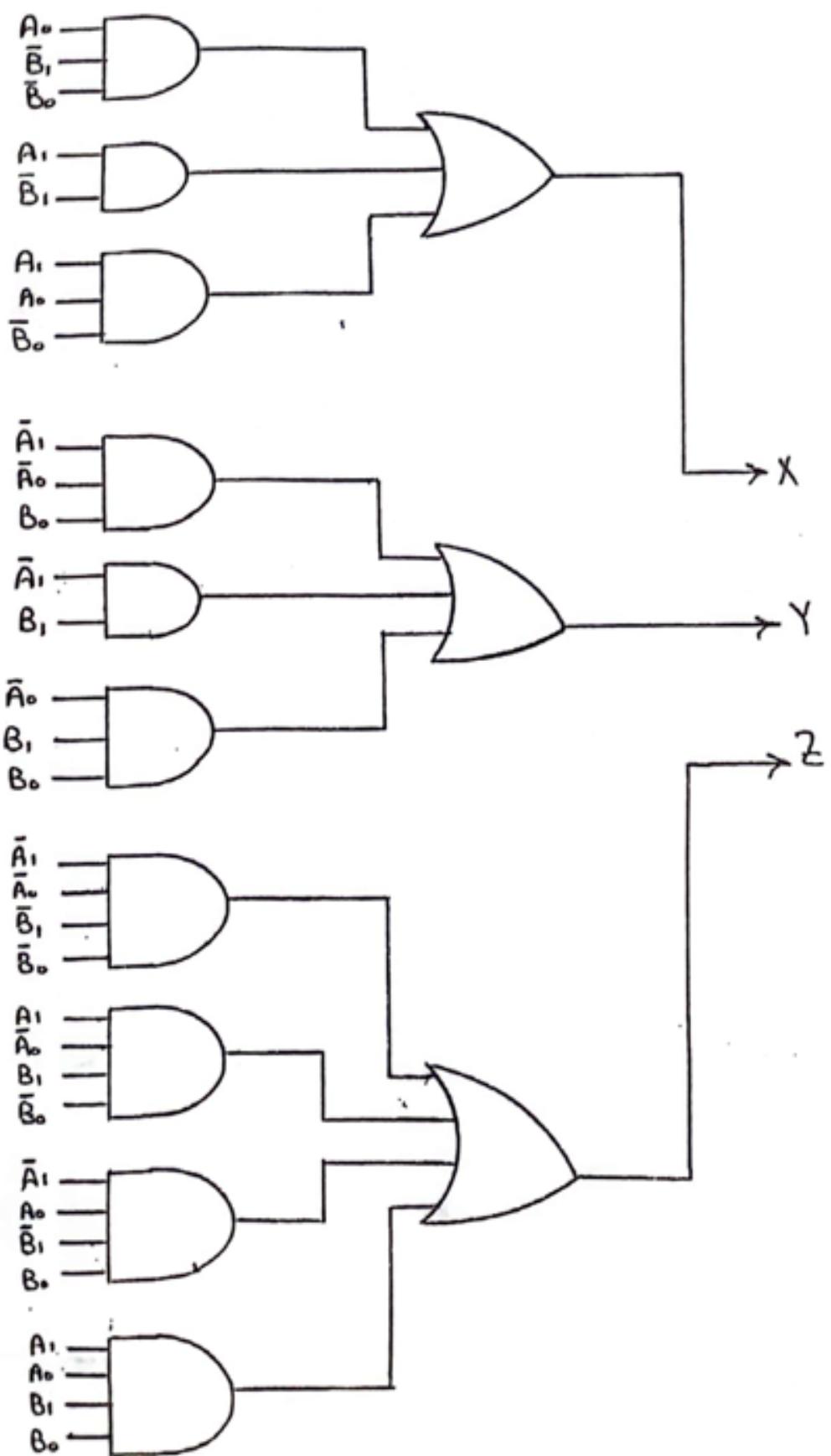
$$Z = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0$$



Note .

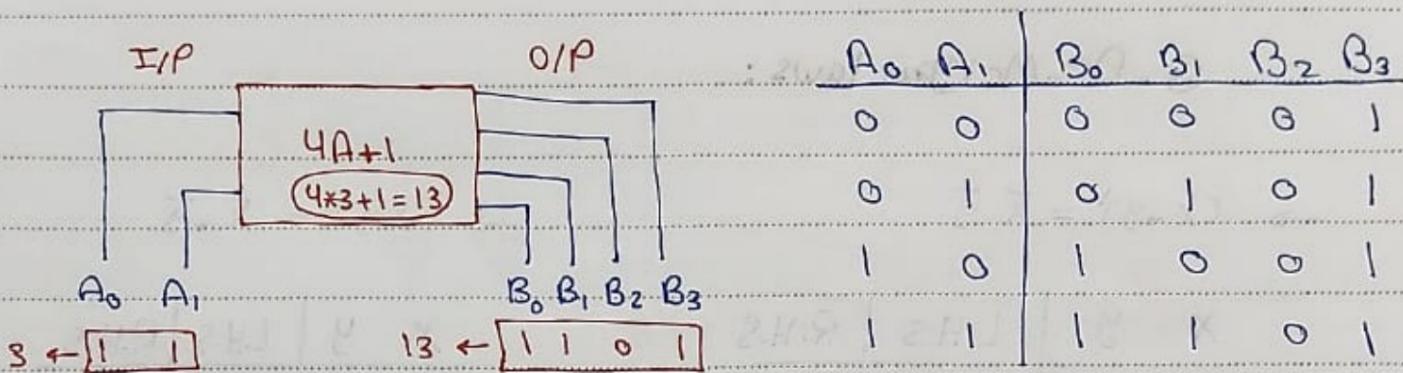i) - A circuit that accepts 2-bit number (A), the output is $(4A+1)$:




$$B_0 = A_0$$


$$B_1 = A_1$$

$$B_2 = 0$$

$$B_3 = 1$$

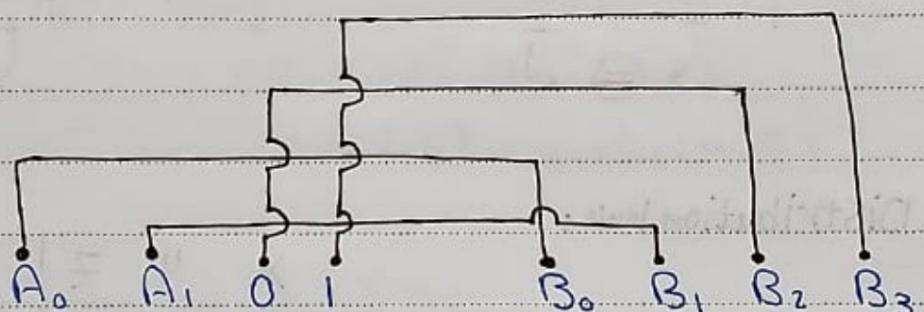

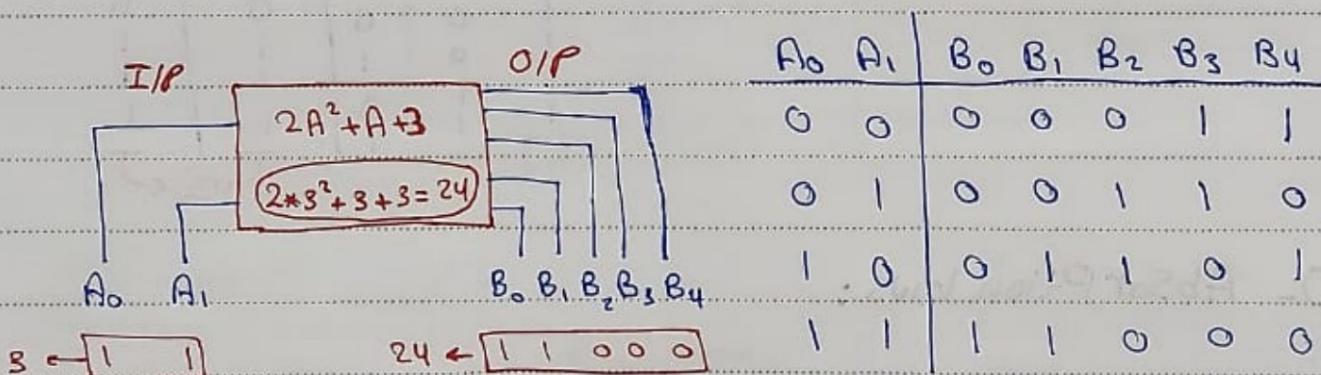j) - A circuit that accepts 2-bit number (A), the output is $(2A^2+A+3)$:




$$B_0 = A_0 \cdot A_1$$

$$B_1 = A_0$$

$$B_2 = A_0 + A_1$$

$$B_3 = \bar{A}_0$$


$$B_4 = \bar{A}_1$$

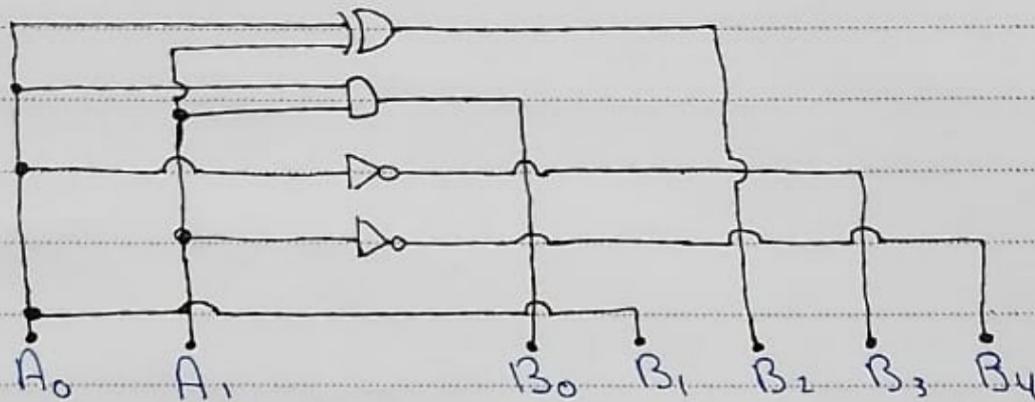

(K)- A circuit that accepts 3-bit number (A), the output is : $(3A + 4)$:

I/P	3A+4	O/P	$A_0 \quad A_1 \quad A_2$	$B_0 \quad B_1 \quad B_2 \quad B_3 \quad B_4$
$A_0 \quad A_1 \quad A_2$	$3A+4$ $3 \times 7 + 4 = 25$	$B_0 \quad B_1 \quad B_2 \quad B_3 \quad B_4$	0 0 0	0 0 1 0 0
7 ← 1 1 1			0 0 1	0 0 1 1 1
			0 1 0	0 1 0 1 0
			0 1 1	0 1 1 0 1
			1 0 0	1 0 0 0 0
			1 0 1	1 0 0 1 1
			1 1 0	1 0 1 1 0
			1 1 1	1 1 0 0 1
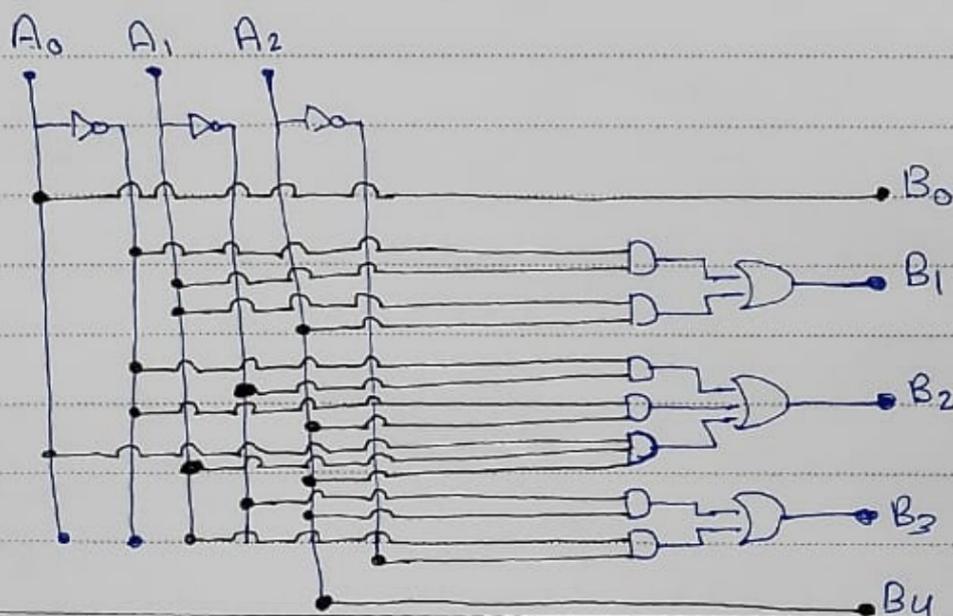
$$B_0 = A_0, \quad B_1 = \bar{A}_0 A_1 + A_1 A_2, \quad B_2 = \bar{A}_0 \bar{A}_1 + \bar{A}_0 A_2 + A_0 A_1 \bar{A}_2, \quad B_3 = \bar{A}_1 A_2 + A_1 \bar{A}_2, \quad B_4 = A_2$$




18. Using Decoder and OR gates, implement the following circuits:

a. Full Adder circuit.

$$C_{out} = m_3 + m_5 + m_6 + m_7$$

$$S = m_1 + m_2 + m_4 + m_7$$


A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

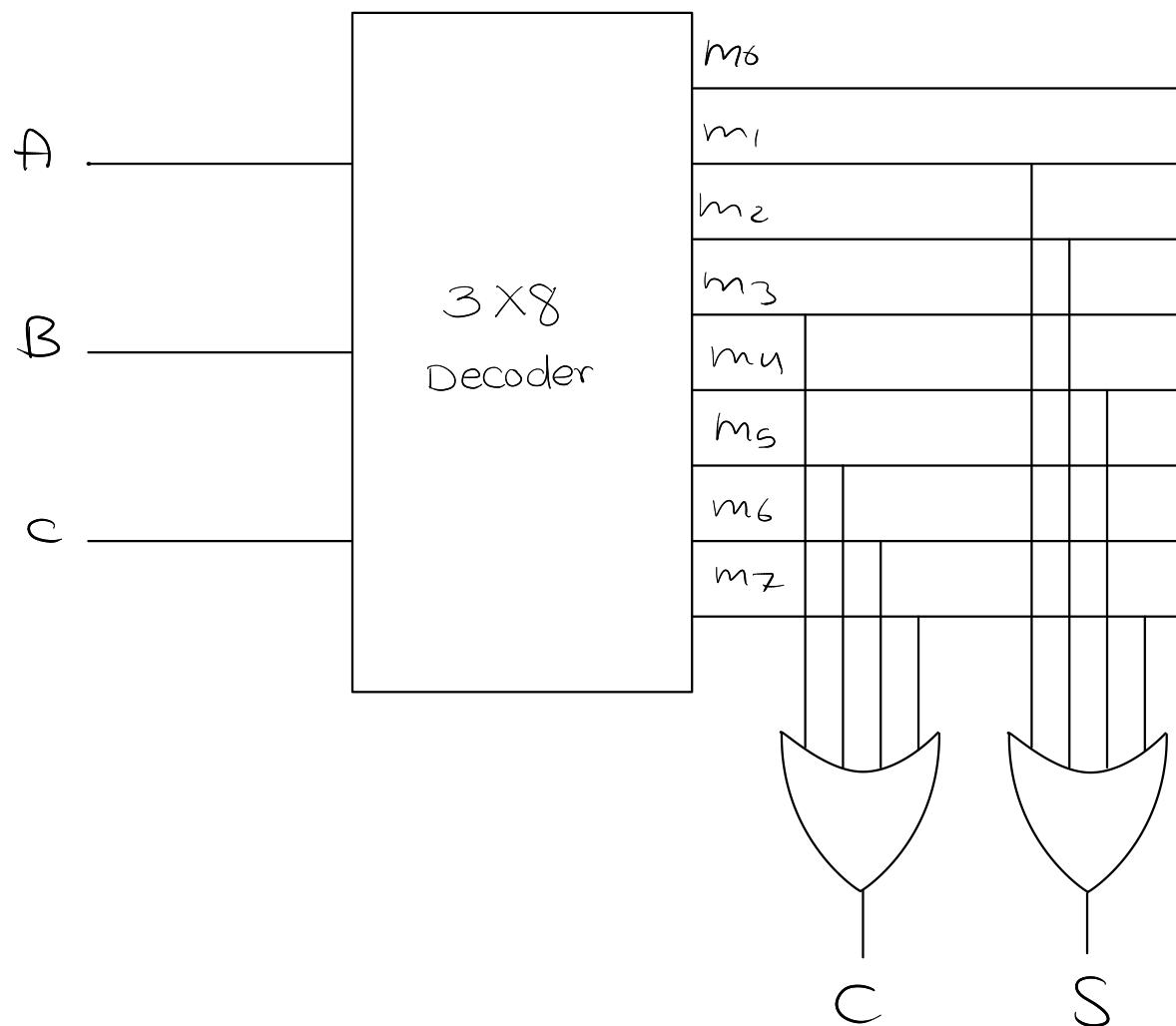

b. $F(A, B, C) = AB' + CA'$


	B	0	0	1	1
	C	0	1		0
A		m_6	m_1	m_2	m_2
0					
1		m_4	m_5		

$$F(A, B, C) = m_1 + m_3 + m_4 + m_5$$

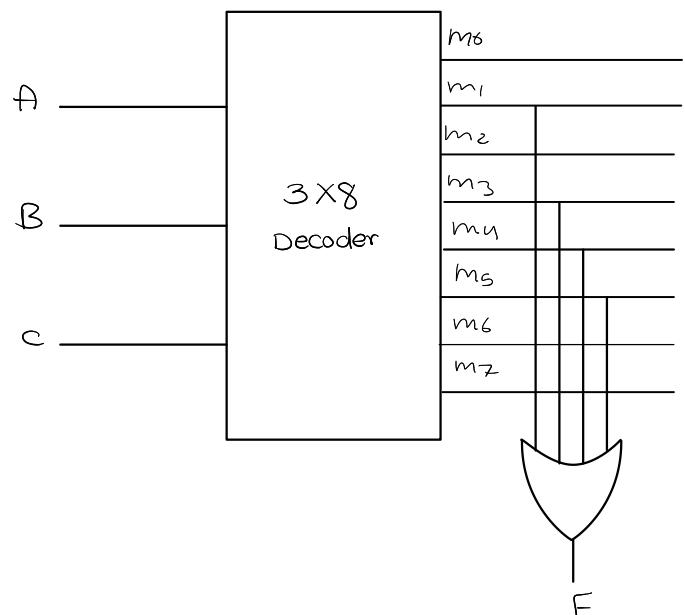


c. $F(A, B, C, D) = A'B + AC' + CD$

	C	0	0	1	1
	D	0	1		0
A		0	1	1	2
0					
0	1	4	5	7	6
1	1	12	13	15	16
1	0	8	9	11	10

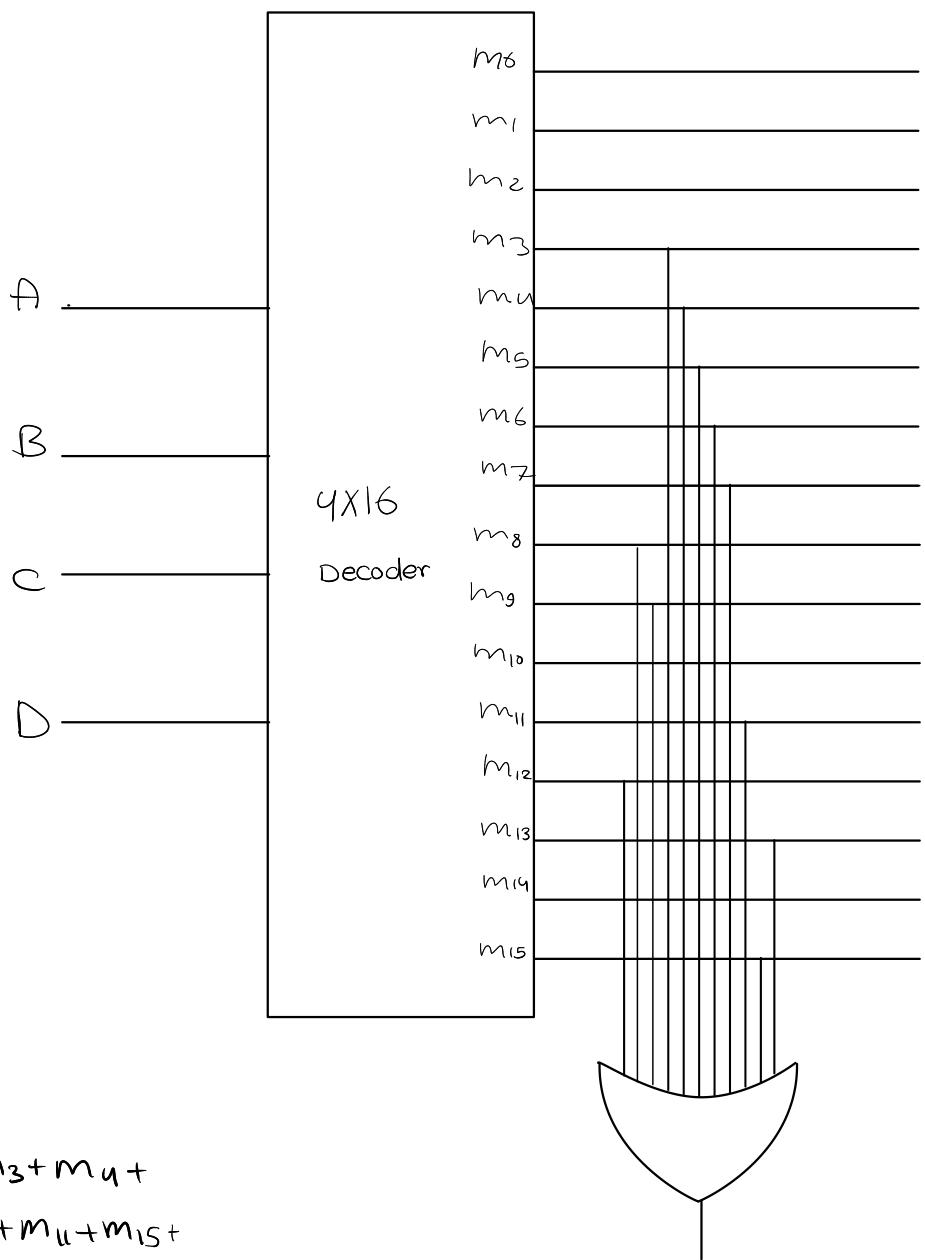


$$F(A, B, C, D) = m_{12} + m_{13} + m_3 + m_4 + m_5 + m_6 + m_7 + m_{11} + m_{15} + m_8 + m_9$$

d. $F(A, B, C) = \sum(0, 3, 4, 5)$.

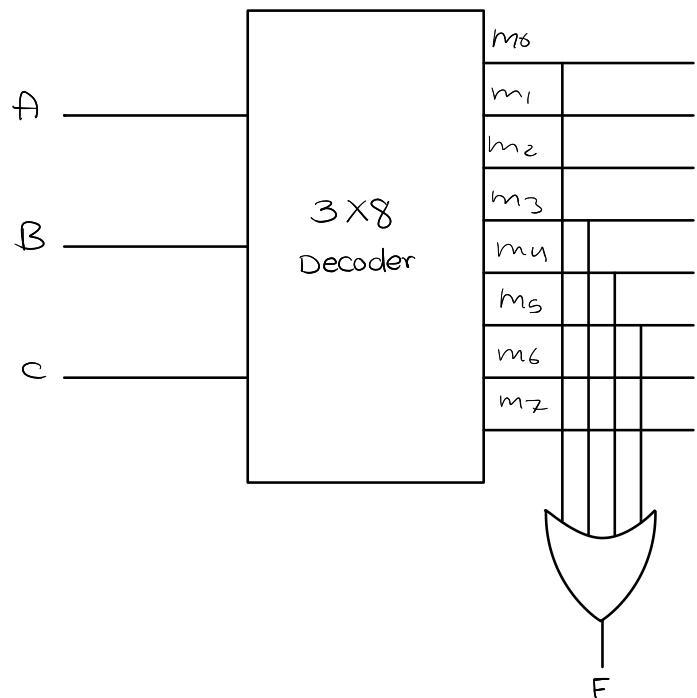


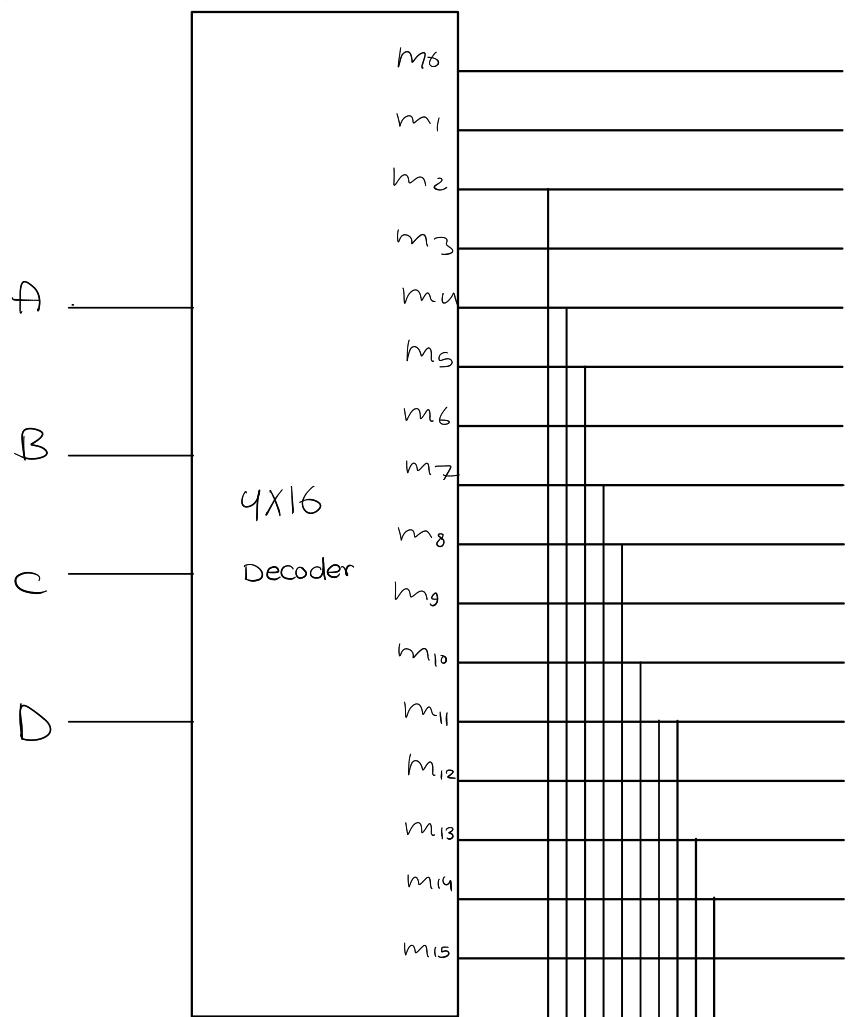f. $F(A, B, C, D) = \prod(0, 1, 3, 6, 9, 12, 15)$.




$$f(A, B, C, D) = m_2 + m_4 + m_5 + m_7 + m_8 + \\ m_{10} + m_{11} + m_{13} + m_{14}$$

g. 2-bit magnitude comparator.

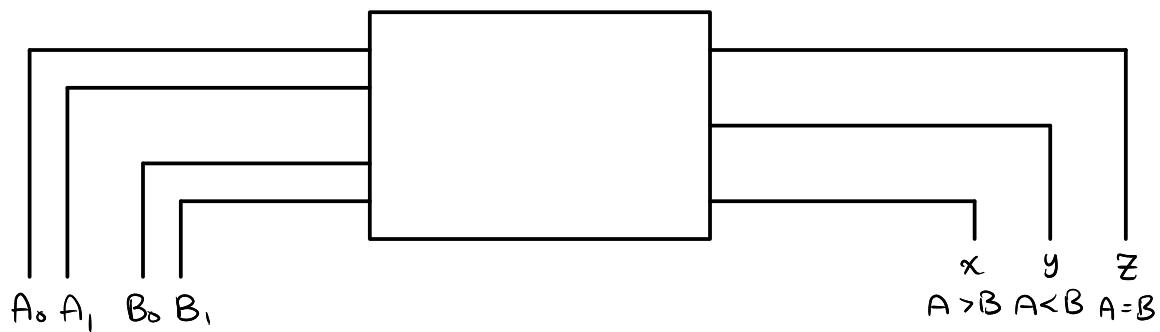


A_1	A_0	B_1	B_0	x	y	z
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	(0)	(0)	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

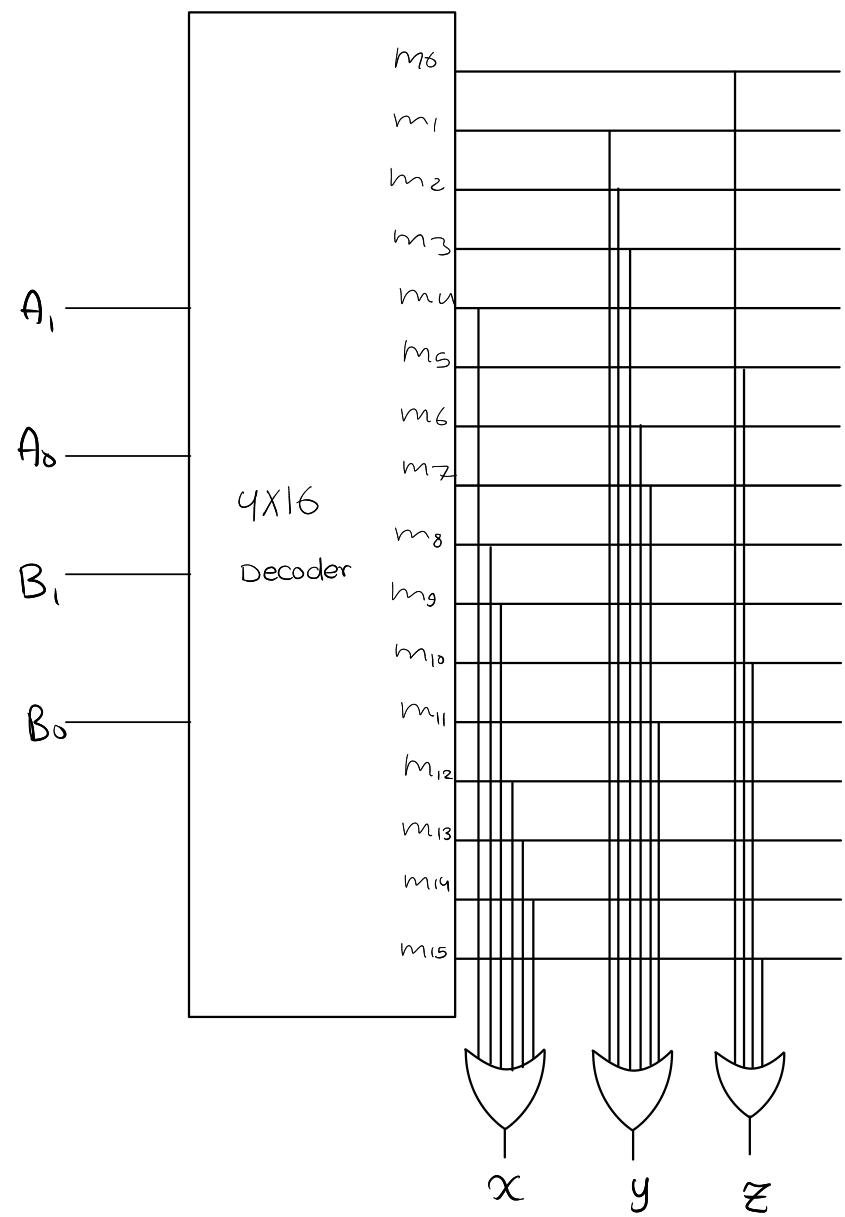

مقدمة
الجامعة
الى

h. A logic circuit that accepts two bit number, then multiply it by 3.

A	B	X	Y	Z	m
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	1	0
1	1	1	0	0	1

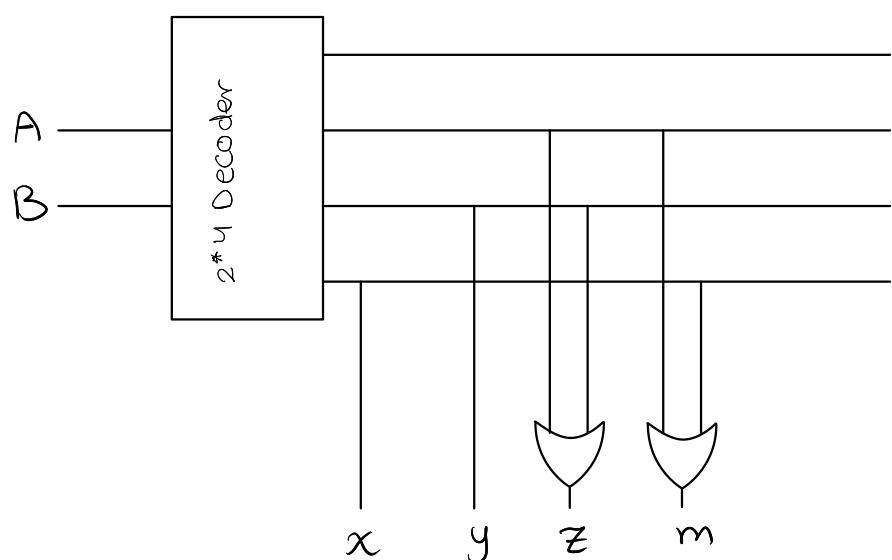


i. A logic circuit that accepts BCD number, then multiply it by 2.

A	B	C	D	X	Y	Z	m	N
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	0	0
0	0	1	1	0	0	1	1	0
0	1	0	0	0	1	0	0	0
0	1	0	1	0	1	0	1	0
0	1	1	0	0	1	0	0	0
0	1	1	1	0	1	0	1	0
1	0	0	0	1	0	0	0	0
1	0	0	1	1	0	0	1	0
1	0	1	0	X	X	X	X	X
1	0	1	1	X	X	X	X	X
1	1	0	0	X	X	X	X	X
1	1	0	1	X	X	X	X	X
1	1	1	0	X	X	X	X	X
1	1	1	1	X	X	X	X	X

$\alpha = m_8 + m_9$
 $y = m_4 + m_5 + m_6 + m_7$
 $z = m_2 + m_3 + m_6 + m_7$
 $m = m_1 + m_3 + m_5 + m_7 + m_9$
 $N = 0$

عایلی دوست Decoder
لینکس کنٹرول

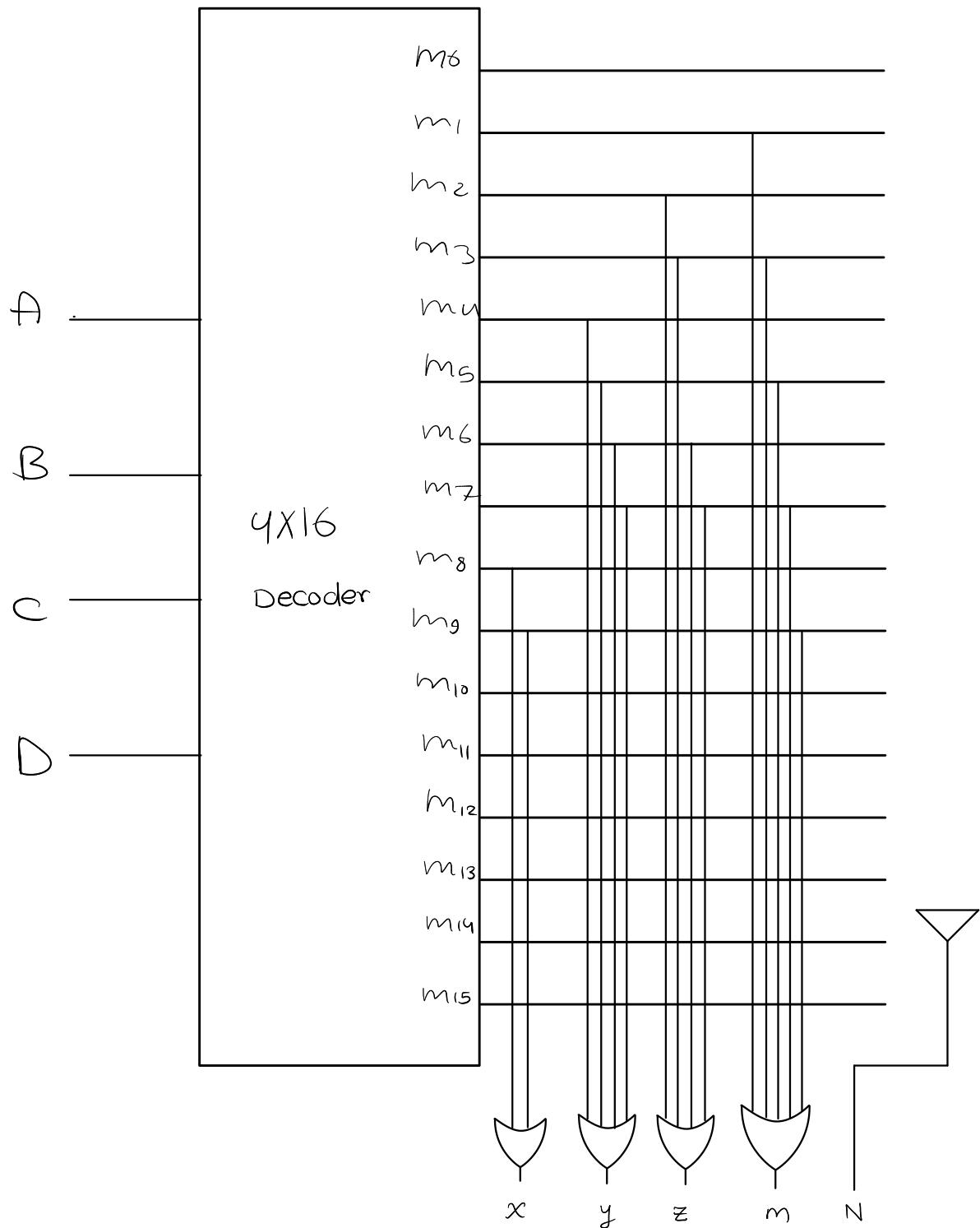


19. Using Decoder and AND gates, implement the following circuits:

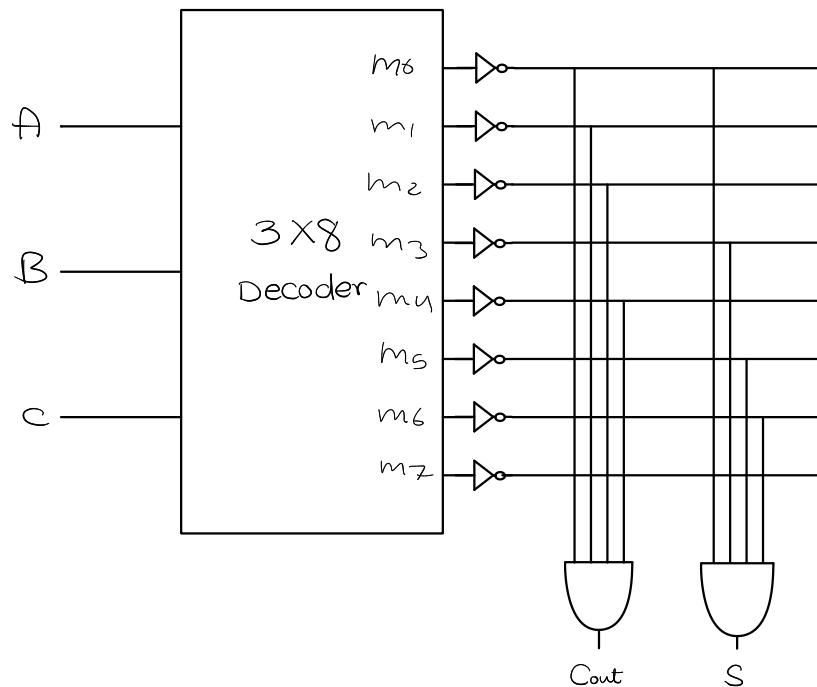a. Full adder circuit.

$$C_{out} = M_0 \cdot M_1 \cdot M_2 \cdot M_4$$

$$S = M_0 \cdot M_3 \cdot M_5 \cdot M_6$$




A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

b. F(A, B, C) = AB' + CA + B'C.


	B	0	0	1	1
A	C	0	1	1	0
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	1	1	

$$F(A, B, C) = M_0 \cdot M_1 \cdot M_3$$

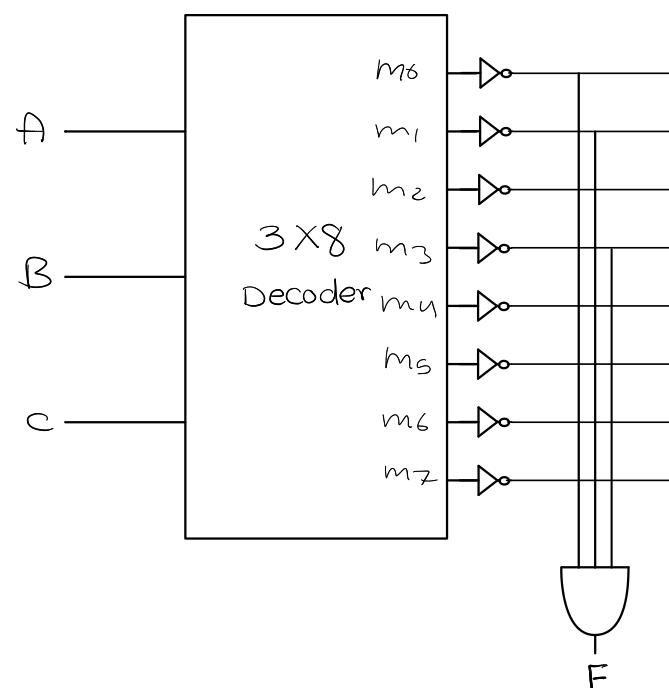


c. $F(A, B, C) = \sum(2, 3, 4, 7)$.

$F(A, B, C) = \prod(0, 1, 5, 6)$

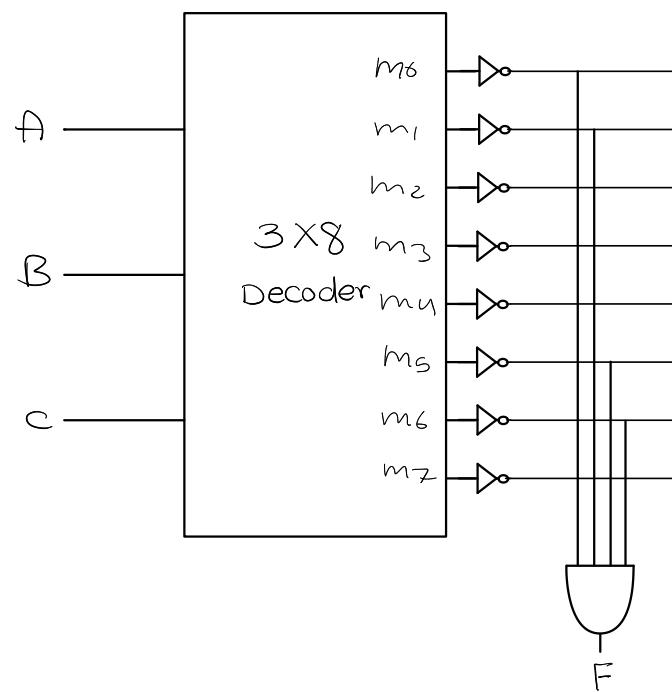


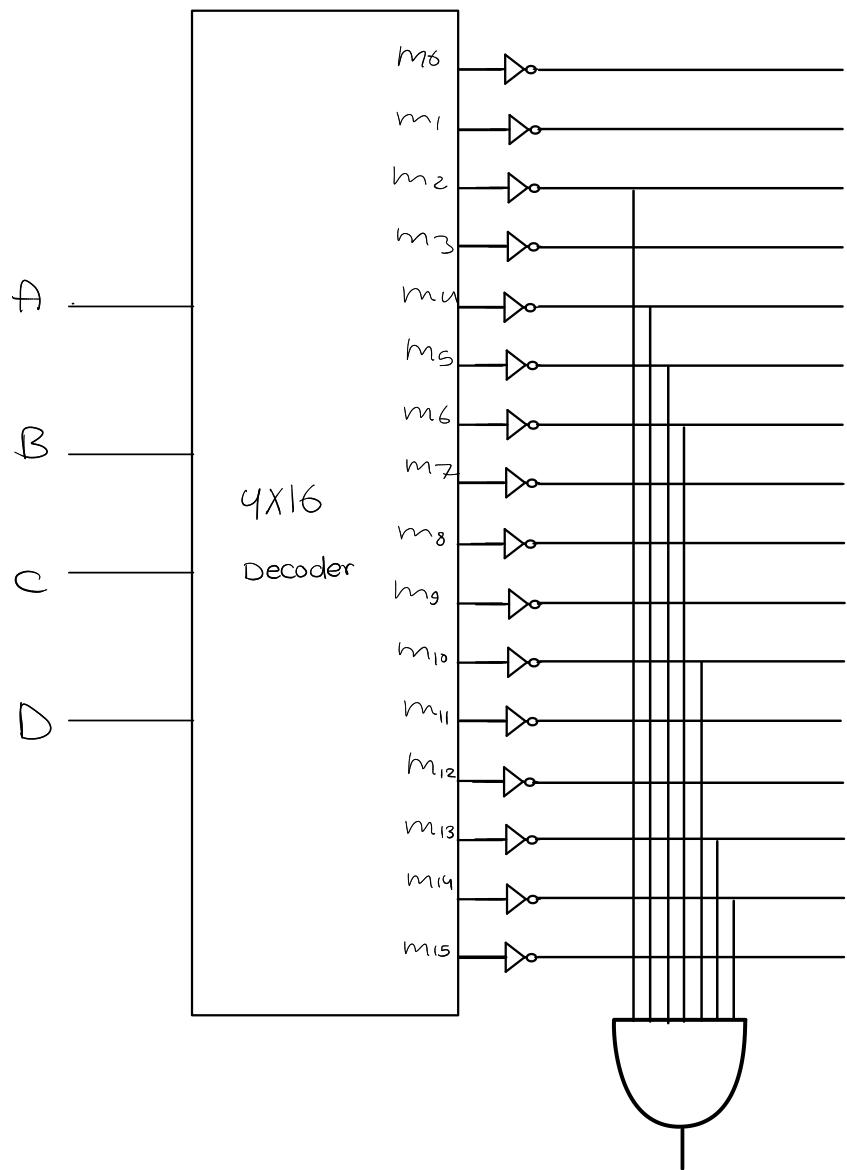d. $F(A, B, C, D) = \prod(2, 4, 5, 6, 10, 13, 14)$.




e. A logic circuit that accepts three bit number, then multiply it by 2.

A	B	X	y	z	m
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	1	0
1	1	1	0	0	1

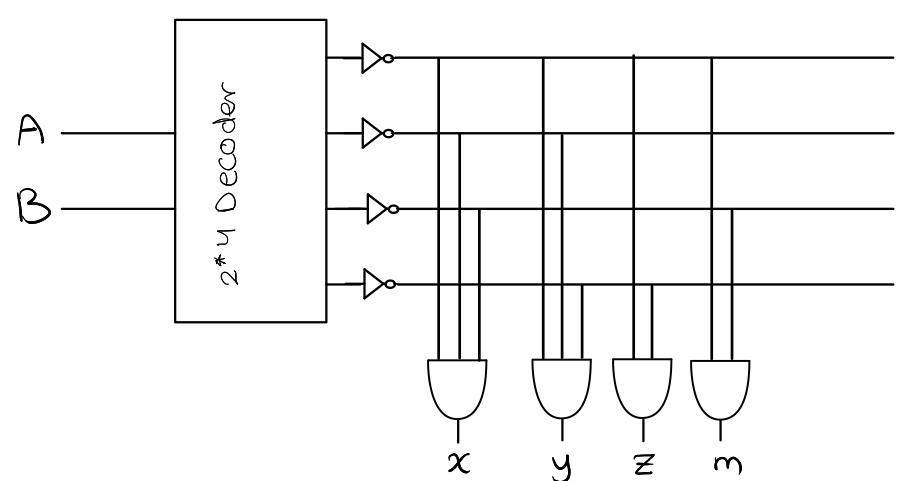

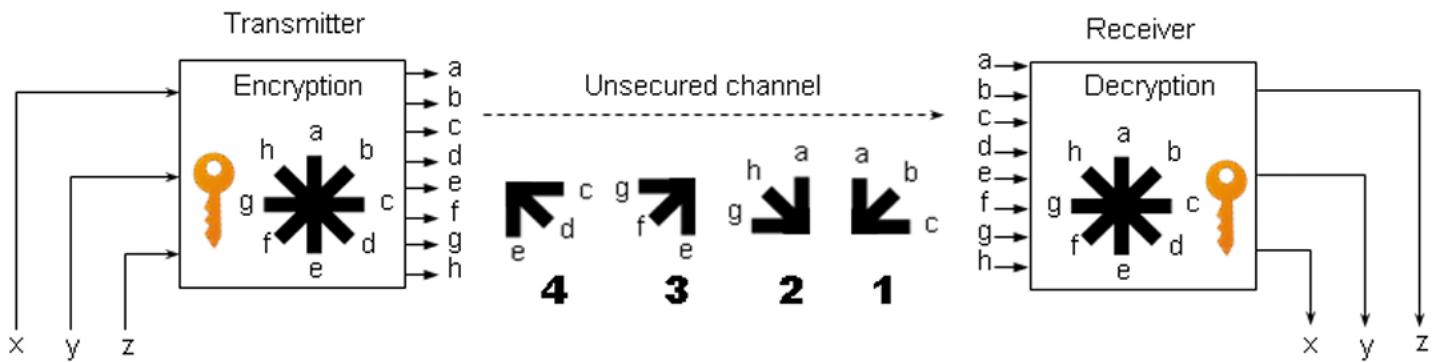21. Dear student, your friend has invented a new encryption technique which he called "Graphical Encryption" as shown below. The data to be encrypted is the numbers "1, 2, 3, 4". However, he needs your help in designing the logic circuits needed at the transmitter and receiver side.



y	0	0	1	1
z	0	1	1	0
x	X	(1)	0	(1)
0	(0)	X	X	X
1	0	X	X	X

$$a = \bar{y}z + \bar{z}y = y \oplus z$$

y	0	0	1	1
z	0	1	1	0
x	X	0	(1)	0
0	(0)	X	(X)	X
1	0	X	X	X

$$e = \bar{y}\bar{z} + yz = y \odot z$$

y	0	0	1	1
z	0	1	1	0
x	X	0	(1)	0
0	(0)	X	(X)	X
1	0	X	X	X

$$F = yz$$

x	y	z	a	b	c	d	e	f	g	h
0	0	0	X	X	X	X	X	X	X	X
0	1	0	(1)	1	1	1	0	0	0	0
1	0	1	0	1	0	0	0	0	0	1
1	1	0	0	0	0	0	1	1	1	0
1	0	1	0	0	0	1	1	1	0	0
1	1	1	X	X	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X	X


$$b = (x+y)'$$

$$c = y'$$

$$d = x$$

$$g = y$$

$$h = (x+z)'$$

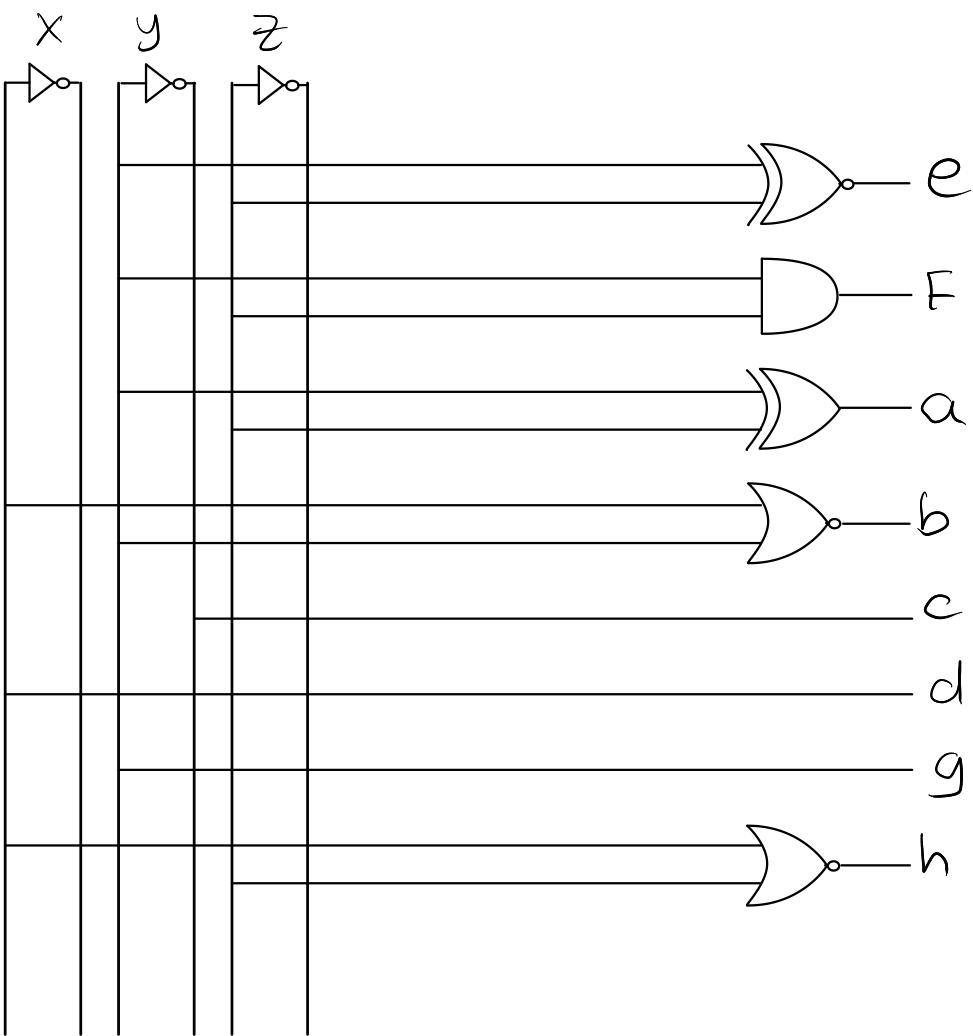

a	b	c	d	e	f	g	h	x	y	z
1	1	1	0	0	0	0	0	0	1	1
1	0	0	0	0	0	1	1	0	0	0
0	0	0	0	1	1	1	0	0	0	1
0	0	1	1	1	0	0	0	1	0	0

عشر عدد الاحوال الممكنة في ما يدخل اصحاب




$$x = \bar{a}\bar{b}c\bar{d}\bar{e}\bar{f}\bar{g}\bar{h}$$

$$y = a\bar{b}\bar{c}\bar{d}\bar{e}\bar{f}gh + \bar{a}\bar{b}\bar{c}\bar{d}ef\bar{g}\bar{h}$$

$$z = abc\bar{d}\bar{e}\bar{f}\bar{g}\bar{h} + \bar{a}\bar{b}\bar{c}def\bar{g}\bar{h}$$

السؤال قبل الآخر
نفس الفكرة والرسالة
أسهل شوية
هنسايش ترسم بعما
روغان أنا ؟

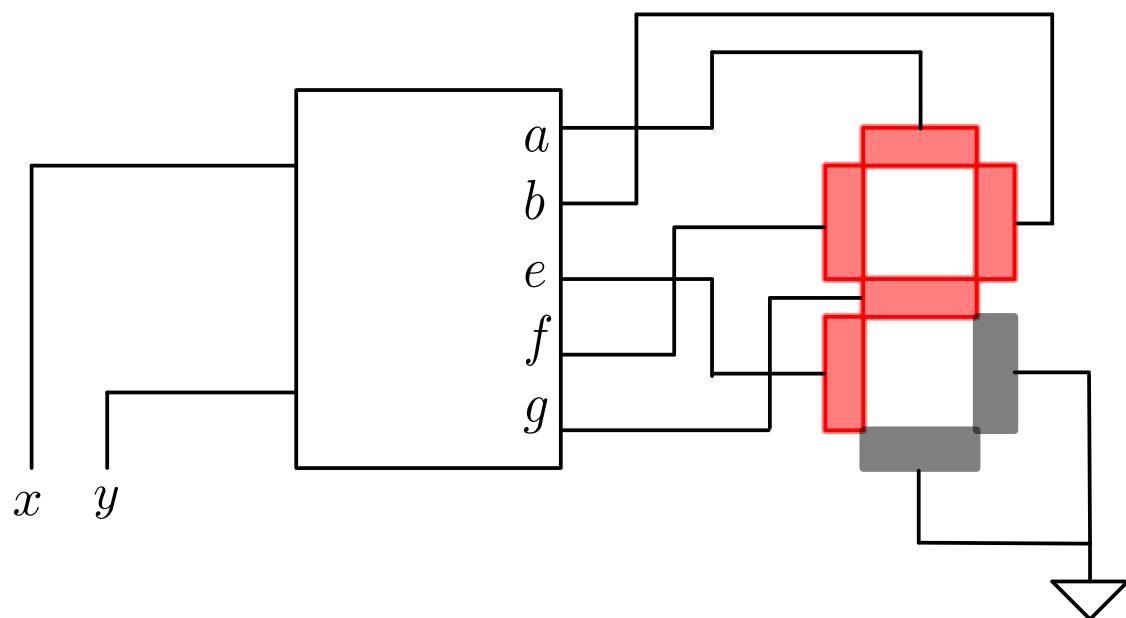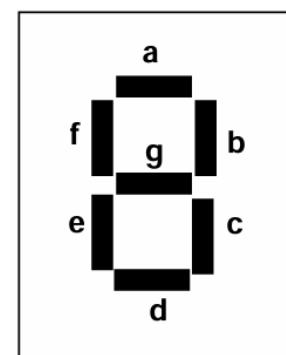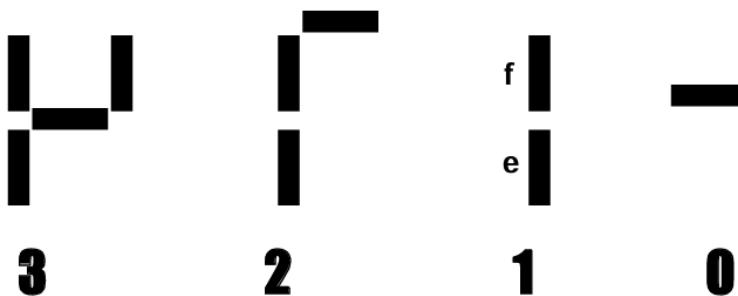
20. Design a digital circuit that accepts 2-bit binary number and the output is the numbers (0, 1, 2, 3) appeared on the seven segments in the Arabic fashion as shown in the following figure. (Note: the only used of the seven segments are the segments (a, b, e, f, g).



Truth table:

x	y	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	1	1	0
1	0	1	0	0	0	1	1	0
1	1	0	1	0	0	1	1	1

Diagram

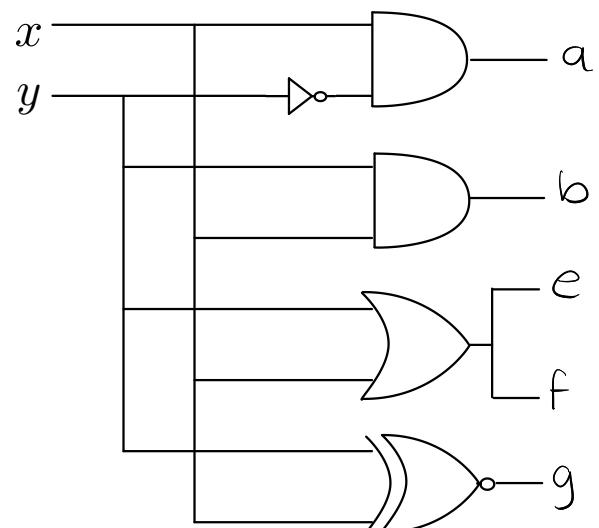

$$a = x\bar{y}$$

✓
∅


x	y	a	b
0	0	0	0
1	0	1	0

$$b = xy$$

$$e = x + y = f$$


$$g = x \oplus y$$

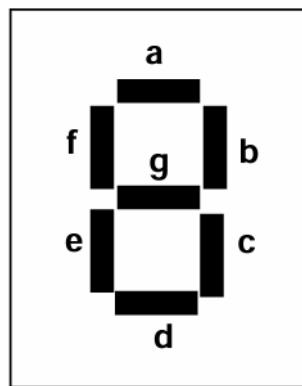22. Design a digital circuit for segment 'g' ONLY of the circuit that accepts BCD number and the output is appeared on the seven segments display.




x	y	z	m	g
0	0	0	0	0
0	1	0	1	0
1	0	1	0	1
1	1	1	1	1
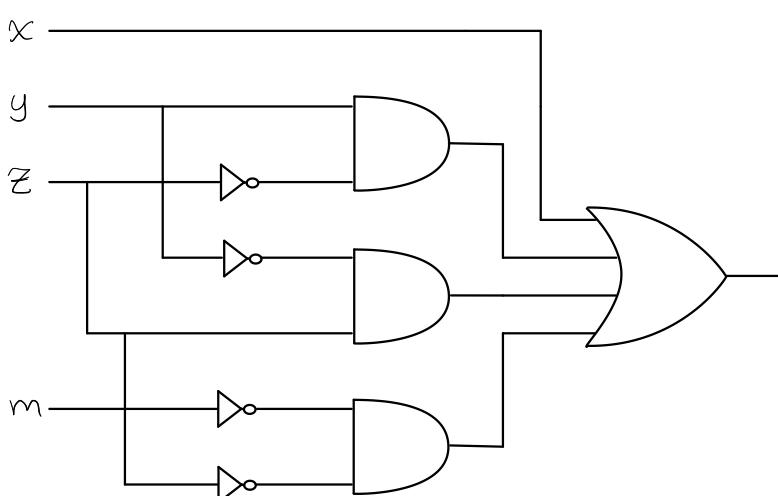
$$g = x + y\bar{z} + \bar{z}m + \bar{y}z$$




x	y	z	m	g
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

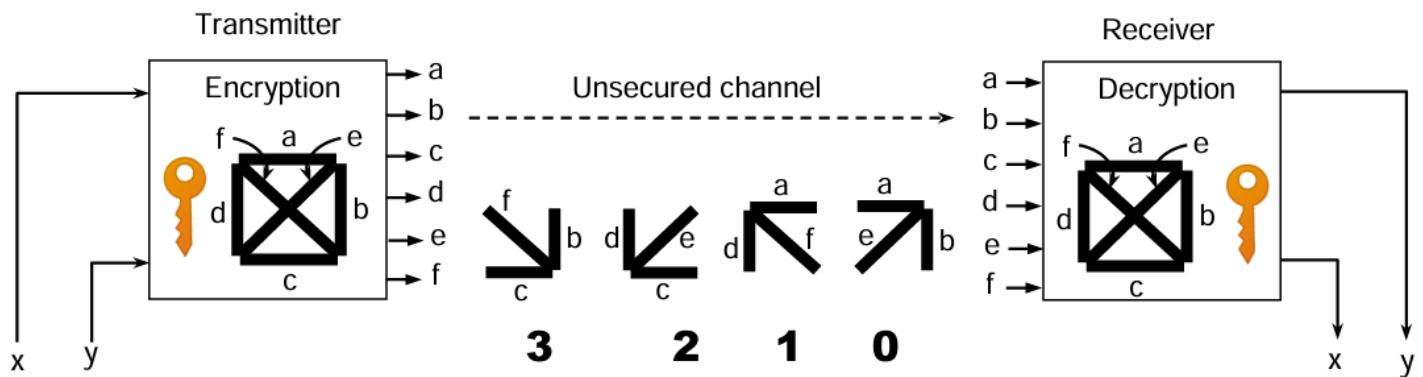23. Dear student, your friend has invented a new encryption technique which he called "Graphical Encryption" as shown below. The data to be encrypted is a two bit number. However, he needs your help in designing the logic circuits needed at the transmitter and receiver side.



x	y	a	b	c	d	e	f
0	0	1	1	0	0	1	0
0	1	1	0	0	1	0	1
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	1
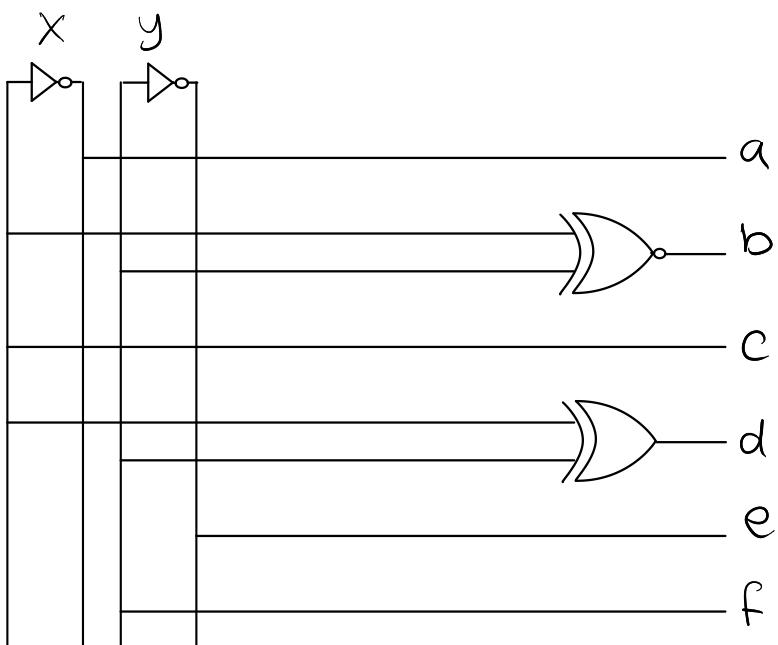
$$\begin{aligned}
 a &= \bar{x} & f &= y \\
 b &= x \odot y & \\
 c &= x & \\
 d &= x \oplus y & \\
 e &= \bar{y}
 \end{aligned}$$




a	b	c	d	e	f	x	y
1	1	0	0	1	0	0	0
1	0	0	1	0	1	0	(1)
0	0	1	1	1	0	(1)	0
0	1	1	0	0	1	(1)	(1)



نحوی x, y فی ترتیب
 \min terms

$$x = \bar{a}\bar{b}cdef + \bar{a}bcd\bar{e}\bar{f}$$
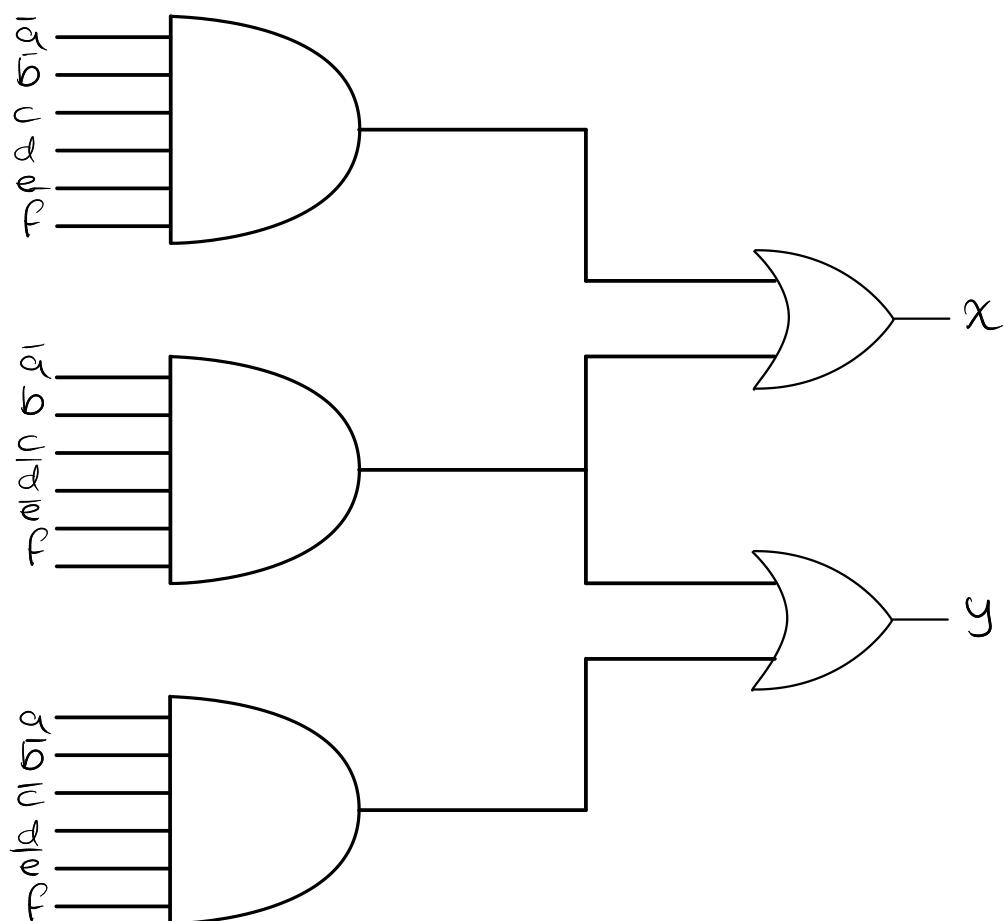
$$y = a\bar{b}\bar{c}def + \bar{a}bc\bar{d}\bar{e}\bar{f}$$




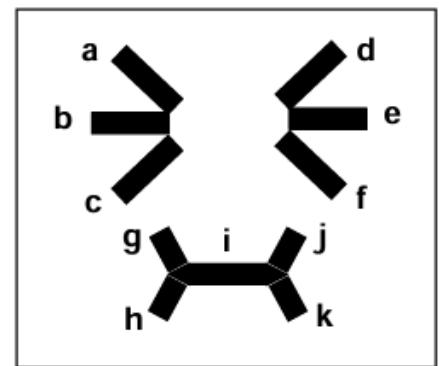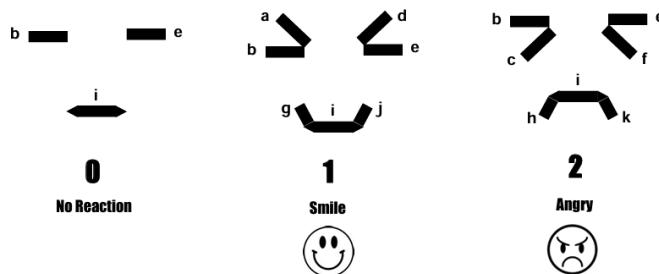24. Design a digital circuit that accepts 2-bit binary number (0, 1, and 2 only) and the output is one of the following impressions (No Reaction, Smile, or Angry) appeared on the nine segments in the shown figures.



x	y	a	b	c	d	e	f	g	h	i	j	k
0	0	0	1	0	0	1	0	0	0	1	0	0
0	1	1	1	0	1	1	0	1	0	1	1	0
1	0	0	1	1	0	1	1	0	1	1	0	1
1	1	X	X	X	X	X	X	X	X	X	X	X

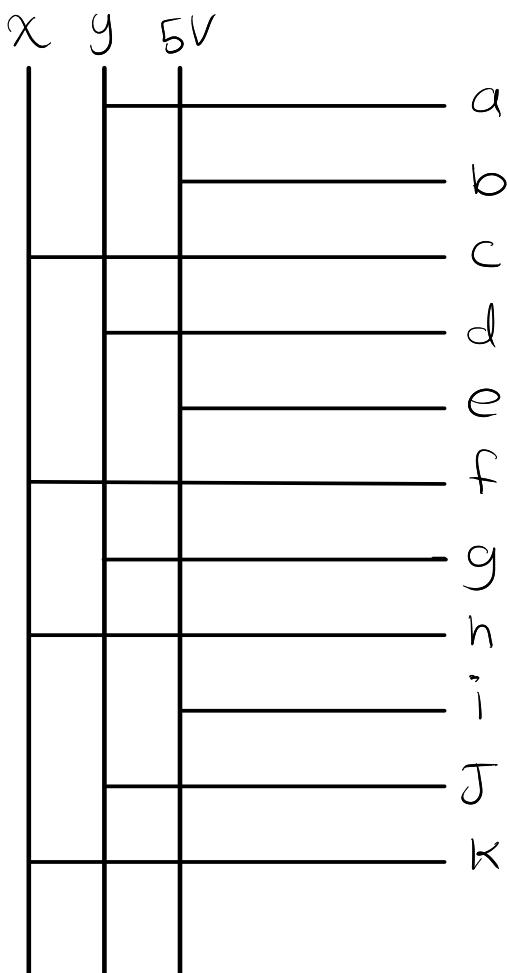Below the table, arrows point to the segments: y points to segment i; 1 points to segment b; x points to segment h; y points to segment g; 1 points to segment d; x points to segment e; y points to segment f; 1 points to segment a; y points to segment c; 1 points to segment j; x points to segment k.



و هكذا نكون قد وصلنا للختام
سائلين المولى لنا و إياكم التوفيق

محمد النوسلاني

مختار